

PART A – DELTA/DELTA TRANSFORMERS

12-2 DELTA TRANSFORMER VOLTAGE

In a delta configured transformer, the line voltage equals the phase voltage ($E_{Line} = E_{Phase}$). Figure 12-11.

Primary Delta Voltage

LINE Voltage	PHASE Voltage
L ₁ to L ₂ = 480V	Phase A winding = 480V
L ₂ to L ₃ = 480V	Phase B winding = 480V
L ₃ to L ₁ = 480V	Phase C winding = 480V

Secondary Delta Voltage

LINE Voltage	PHASE Voltage	NEUTRAL Voltage
L ₁ to L ₂ = 240V	Phase A winding = 240V	Neutral to L ₁ = 120V
L ₂ to L ₃ = 240V	Phase B winding = 240V	Neutral to L ₂ = 208V
L ₃ to L ₁ = 240V	Phase C winding = 240V	Neutral to L ₃ = 120V

12-3 DELTA HIGH-LEG

The term high-leg, wild leg or bastard leg is used to identify the conductor of a delta configured system that has a voltage rating of 208V to ground. The high-leg voltage is the vector sum of the voltage of transformers A and C₁, or transformers B and C₂, which equal $120V \times 1.732 = 208V$ for a 120/240V secondary.

Note: The actual voltage is often less than the nominal system voltage because of voltage drop. Figure 12-12.

High-leg Voltage

What is the actual high-leg voltage if the delta configured secondary is 115/230V, 3Ø?

- (a) 115V
- (b) 230V
- (c) 199V
- (d) 240V

• Answer: (c) 199V

$$115V \times 1.732 = 199.18 V$$

12-4 DELTA LINE CURRENTS

In a delta configured transformer, the line current does not equal the phase current.

The line current of a 3Ø transformer can be calculated by the formula:

$$I_{Line} = \frac{VA_{Line}}{E_{Line} \times \sqrt{3}}$$

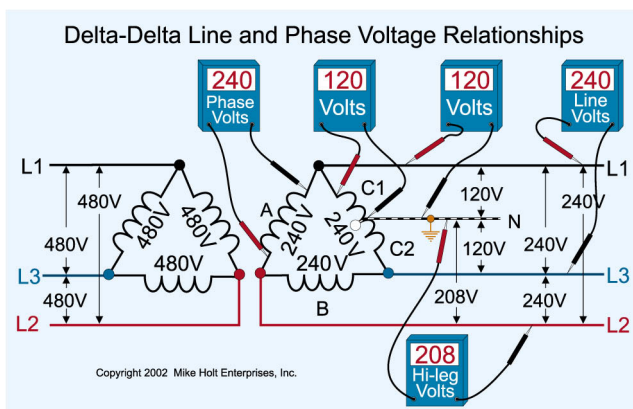


Figure 12-11

Delta-Delta Line and Phase Voltage Relationships

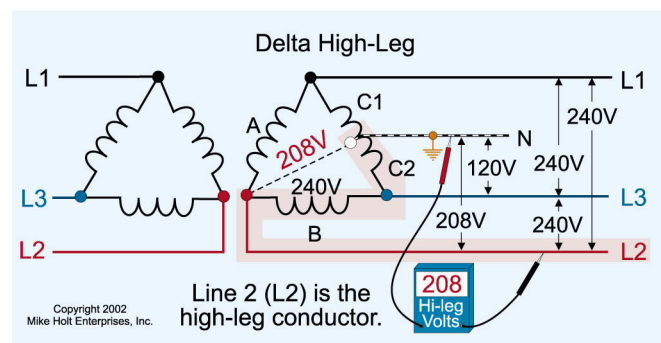


Figure 12-12

Delta High-Leg