

# Table of Contents

## Chapter 3 Basic Electrical Circuits

### Unit 10 Series Circuits

10.0 Introduction .....	131
10.1 Practical Uses of the Series Circuit.....	131
10.2 Understanding Series Calculations .....	132
10.3 Series Circuit Calculations.....	135
10.4 Power Calculations .....	136
10.5 Variations .....	136
10.6 Series Circuit Notes .....	136
10.7 Series-Connected Power Supplies .....	136
Unit 10–Summary.....	138
Unit 10–Conclusion .....	140
Unit 10–Practice Questions.....	141

### Unit 11 Parallel Circuits

11.0 Introduction .....	143
11.1 Practical Uses of the Parallel Circuits .....	143
11.2 Understanding Parallel Calculations .....	145
11.3 Circuit Resistance .....	146
11.4 Parallel Circuit Notes .....	148
11.5 Parallel-Connected Power Supplies .....	149
Unit 11–Summary.....	150
Unit 11–Conclusion .....	152
Unit 11–Practice Questions.....	153

### Unit 12 Series-Parallel Circuits

12.0 Introduction .....	155
12.1 Review of Series and Parallel Circuits .....	155
12.2 Working With Series-Parallel Circuits .....	156
12.3 Voltage .....	157
Unit 12–Summary.....	158
Unit 12–Conclusion .....	159
Unit 12–Practice Questions.....	160

### Unit 13 Multiwire Circuits

13.0 Introduction .....	161
13.1 Neutral Conductor .....	161
13.2 Grounded Conductor .....	162
13.3 Current Flow on the Grounded (Neutral) Conductor .....	162
13.4 Balanced Systems .....	163
13.5 Unbalanced Current.....	163
13.6 Multiwire Branch Circuits .....	165
13.7 Dangers of Multiwire Circuits.....	166
13.8 <i>NEC</i> Requirements.....	167
Unit 13–Summary.....	169
Unit 13–Conclusion .....	171
Unit 13–Practice Questions.....	172
<i>Chapter 3–Final Exam</i> .....	175

## Chapter 4 Electrical Systems and Protection

### Unit 14 The Electrical System

14.0 Introduction .....	183
14.1 Current Flow.....	183
14.2 Utility Neutral Current Path .....	183
14.3 Utility Ground-Fault Current Path .....	184
14.4 Premises Neutral Current Path.....	184
14.5 Premises Ground-Fault Current Path .....	185
14.6 Utility High-Voltage Transmission Lines.....	185
14.7 Conductor Voltage Drop .....	185
14.8 Conductor Power Loss .....	186
14.9 Reducing Voltage Drop and Power Loss.....	187
14.10 Generating Plants .....	187
14.11 Step-Up Substation at Generating Plant.....	187
14.12 Transmission Line .....	188
14.13 Step-Down Substation.....	188

14.14 Primary Distribution Feeders .....188  
 14.15 Distribution Transformer .....188  
 14.16 Secondary Distribution Line .....189  
 Unit 14–Summary.....190  
 Unit 14–Conclusion .....192  
 Unit 14–Practice Questions.....193

**Unit 15 Protection Devices**

15.0 Introduction .....197  
**Part A—Overcurrent Protection Devices** .....197  
 15.1 Overcurrent Protection .....197  
 15.2 Clearing Faults .....198  
 15.3 Overcurrent Protection Device Types .....199  
 15.4 Fuse.....199  
 15.5 Circuit Breaker Trip Elements .....200  
 15.6 Circuit Breaker Types .....200  
 15.7 Available Short-Circuit Current.....201  
 15.8 Interrupting Rating .....201  
 15.9 Short-Circuit Current Rating .....202  
 15.10 Current-Limiting Protection.....203  
**Part B—Ground-Fault Circuit Interrupters** .....203  
 15.11 How a GFCI Works .....203  
 15.12 Neutral-to-Case Detection .....204  
 15.13 Line-to-Neutral Shock Hazard .....204  
 15.14 GFCI Fails—Circuit Remains Energized.....205  
 15.15 GFCI Test Button .....205  
**Part C—Arc-Fault Circuit Interrupters** .....205  
 15.16 Arcing Definition .....205  
 15.17 Series Versus Parallel Arc .....206  
 15.18 AFCI and the *NEC* .....206  
 15.19 AFCI—How They Operate .....207  
**Part D—Ground- Fault Protection of Equipment** .....207  
 15.20 Ground-Fault Protection of Equipment  
 Definition .....207  
 Unit 15–Summary.....208  
 Unit 15–Conclusion .....212  
 Unit 15–Practice Questions.....213  
**Chapter 4–Final Exam**.....219