

# UNIT 12

## OHM'S LAW

### 12.1 Introduction


To understand electrical circuits, you must understand electrical terminology. In this unit you will learn:

- ▶ what electromotive force, intensity, and resistance are
- ▶ what voltmeters, ammeters, and ohmmeters are
- ▶ how to use the Ohm's Law formula

### 12.7 Ohm's Law Formula Circle

To determine which formula in the Ohm's Law Formula Circle to use, place your finger on the unknown value for which you are looking. The two remaining variables "show" you the formula to be used.

▶Figure 12-12

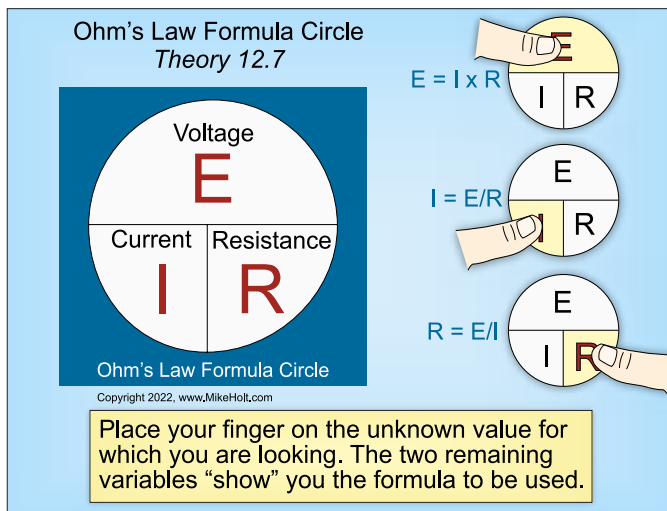


▶Figure 12-12

### ▶ Electromotive Force $E = I \times R$ Example

**Question:** The voltage to a  $192\Omega$  resistor carrying  $0.625A$  is \_\_\_\_\_. ▶Figure 12-13

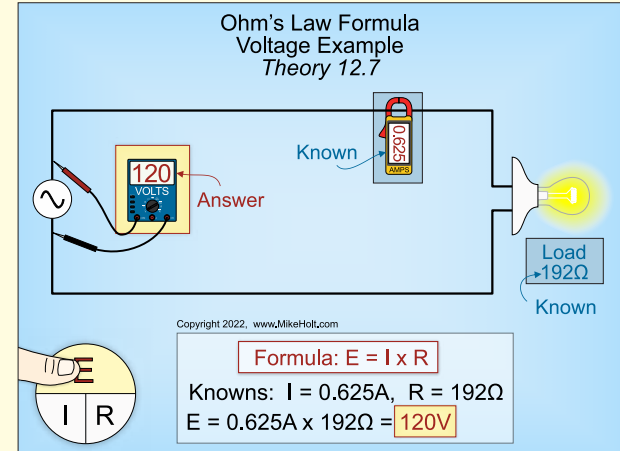- (a) 1V      (b) 110V      (c) 120V      (d) 125V



▶Figure 12-13

**Solution:**

The voltage of this circuit is determined by the formula  $E = I \times R$ .

$$E = I \times R$$

$$I = 0.625A$$

$$R = 192\Omega$$


$$E = 0.625A \times 192\Omega$$

**Answer:** (c) 120V

► Intensity  $I = E/R$  Example

**Question:** If a 120V source supplies a  $192\Omega$  light bulb, the current flow in the circuit will be \_\_\_\_\_. ►Figure 12-14

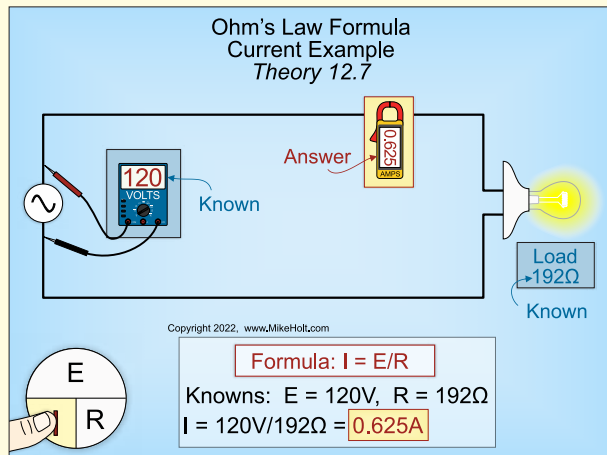- (a) 0.525A    (b) 0.625A    (c) 1.30A    (d) 2.50A



►Figure 12-14

**Solution:**

**Step 1:** What is the question? What is "I"?

**Step 2:** What do you know?

Voltage ( $E$ ) = 120V

Resistance ( $R$ ) =  $192\Omega$

**Step 3:** The formula to use is  $I = E/R$ .

**Step 4:** The answer is  $I = 120V/192\Omega$ .


**Step 5:** The answer is  $I = 0.625A$ .

**Answer:** (b) 0.625A

► Resistance  $R = E/I$  Example

**Question:** The resistance of an incandescent light bulb rated 120V drawing 0.625A is \_\_\_\_\_. ►Figure 12-15

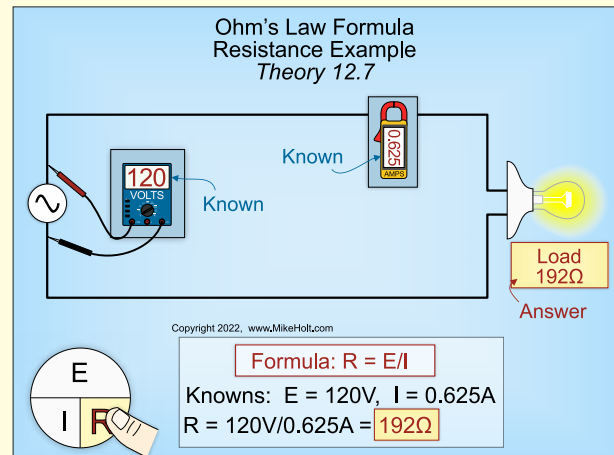- (a)  $100\Omega$     (b)  $175\Omega$     (c)  $192\Omega$     (d)  $200\Omega$



►Figure 12-15

**Solution:**

**Step 1:** What is the question? What is "R"?

**Step 2:** What do you know?

Voltage ( $E$ ) = 120V

Current ( $I$ ) = 0.625A

**Step 3:** The formula to use is  $R = E/I$ .

**Step 4:** The answer is  $R = 120V/0.625A$ .

**Step 5:** The answer is  $R = 192\Omega$ .

**Answer:** (c)  $192\Omega$