



# Table of Contents

## UNIT 1—ELECTRICIAN'S MATH AND BASIC ELECTRICAL FORMULAS

Introduction	1
<b>PART A—ELECTRICIAN'S MATH</b>	1
Introduction	1
1.1 Whole Numbers	1
1.2 Decimal	1
1.3 Fractions	1
1.4 Percentages	2
1.5 Multiplier	2
1.6 Percent Increase	2
1.7 Reciprocals	3
1.8 Squaring a Number	3
1.9 Square Root	4
1.10 Volume	5
1.11 Kilo	5
1.12 Rounding Off	5
1.13 Parentheses	6
1.14 Testing Your Answer for Reasonableness	6
<b>PART B—BASIC ELECTRICAL FORMULAS</b>	7
Introduction	7
1.15 Electrical Circuit	7
1.16 Power Source	7
1.17 Conductance	8
1.18 Circuit Resistance	8
1.19 Ohm's Law	9
1.20 Ohm's Law and Alternating Current	9
1.21 Ohm's Law Formula Circle	9
1.22 PIE Formula Circle	11
1.23 Formula Wheel	12
1.24 Using the Formula Wheel	12
1.25 Power Losses of Conductors	13
1.26 Cost of Power	14
1.27 Power Changes with the Square of the Voltage	14
<b>PART C—BASIC ELECTRIC METERS</b>	16
Introduction	16
1.28 Voltmeter	16

1.29 DC Voltmeter	16
1.30 DC Ammeter	17
1.31 Clamp-on AC Ammeter	17
1.32 Ohmmeters	18
1.33 Wheatstone Bridge	18
1.34 Megohmmeter	18
Conclusion	19

## UNIT 2—ELECTRICAL CIRCUITS

Introduction	49
<b>PART A—SERIES CIRCUITS</b>	49
Introduction	49
2.1 Practical Uses of the Series Circuit	49
2.2 Understanding Series Calculations	51
2.3 Series Circuit Calculations	53
2.4 Power Calculations	53
2.5 Variations	53
2.6 Series Circuit Notes	53
2.7 Series-Connected Power Supplies	54
<b>PART B—PARALLEL CIRCUITS</b>	54
Introduction	54
2.8 Practical Uses of the Parallel Circuit	55
2.9 Understanding Parallel Calculations	56
2.10 Circuit Resistance	57
2.11 Parallel Circuit Notes	59
2.12 Parallel-Connected Power Supplies	59
<b>PART C—SERIES-PARALLEL CIRCUITS</b>	59
Introduction	59
2.13 Review of Series and Parallel Circuits	60
2.14 Working Series-Parallel Circuits	60
2.15 Voltage	61
<b>PART D—MULTIWIRE BRANCH CIRCUITS</b>	62
Introduction	62
2.16 Neutral Conductor	62
2.17 Grounded Conductor	62

2.18	Current Flow on the Grounded Neutral Conductor .....	63
2.19	Balanced Systems .....	64
2.20	Unbalanced Current.....	64
2.21	Multiwire Branch Circuit .....	65
2.22	Dangers of Multiwire Circuits .....	66
2.23	NEC Requirements.....	67
	Conclusion .....	68

### UNIT 3—UNDERSTANDING ALTERNATING CURRENT .....

Introduction .....	97
--------------------	----

#### PART A—UNDERSTANDING ALTERNATING CURRENT .....

Introduction .....	97	
3.1	Current Flow.....	97
3.2	Why Alternating Current is Used.....	98
3.3	How Alternating Current is Produced.....	98
3.4	AC Generator.....	98
3.5	Waveform .....	99
3.6	Sine Wave .....	99
3.7	Nonsymmetrical Waveform.....	100
3.8	Frequency .....	100
3.9	Phase.....	101
3.10	Degrees .....	101
3.11	Lead or Lag .....	101
3.12	Values of Alternating Current.....	101

#### PART B—CAPACITANCE .....

Introduction .....	102	
3.13	Charged Capacitor.....	102
3.14	Electrical Field .....	103
3.15	Discharging a Capacitor .....	103
3.16	Determining Capacitance .....	103
3.17	Uses of Capacitors.....	104
3.18	Phase Relationship .....	105

#### PART C—INDUCTION .....

Introduction .....	105	
3.19	Self-Induction.....	106
3.20	Induced Voltage and Applied Current .....	106
3.21	Conductor AC Resistance.....	106
3.22	Impedance.....	107
3.23	Conductor Shape .....	107
3.24	Magnetic Cores.....	108
3.25	Self-Induced and Applied Voltage.....	109
3.26	Current Flow.....	109
3.27	Phase Relationship .....	109
3.28	Uses of Induction .....	110

#### PART D—POWER FACTOR.....

Introduction .....	110	
3.29	Apparent Power (Volt-Amperes).....	110
3.30	True Power (Watts).....	111
3.31	Power Factor.....	111
3.32	Unity Power Factor.....	112
3.33	Power Factor Formulas.....	112
3.34	Cost of True Power.....	113
3.35	Effects of Power Factor.....	113

#### PART E—EFFICIENCY .....

Introduction .....	114	
3.36	Efficiency Formulas.....	115
Conclusion.....	117	

### UNIT 4—MOTORS AND TRANSFORMERS.....

Introduction .....	151
--------------------	-----

#### PART A—MOTORS .....

Introduction .....	151	
4.1	Motor Principles .....	152
4.2	Dual-Voltage AC Motors .....	152
4.3	Motor Horsepower Rating .....	152
4.4	Motor Current Ratings .....	153
4.5	Calculating Motor FLA.....	153
4.6	Motor-Starting Current.....	154
4.7	Motor-Running Current.....	155
4.8	Motor Locked-Rotor Current (LRC).....	155
4.9	Motor Overload Protection.....	155
4.10	Direct-Current Motor Principles .....	155
4.11	Direct-Current Motor Types .....	156
4.12	Reversing the Rotation of a DC Motor .....	156
4.13	AC Induction Motor .....	156
4.14	Alternating-Current Motor Types.....	157
4.15	Reversing the Rotation of an AC Motor .....	157

#### PART B—TRANSFORMERS .....

Introduction .....	158	
4.16	Transformer Basics .....	158
4.17	Secondary Induced Voltage .....	158
4.18	Autotransformers.....	159
4.19	Power Losses .....	159
4.20	Harmonic Current.....	161
4.21	Efficiency.....	161
4.22	Transformer Turns Ratio .....	161
4.23	Transformer kVA Rating .....	163
4.24	Current Flow.....	163
4.25	Current Rating .....	163
Conclusion.....	164	

## UNIT 5—RACEWAY AND BOX CALCULATIONS.....193

Introduction .....193

### PART A—RACEWAY FILL.....193

5.1 Understanding the NEC, Chapter 9 Tables .....193

5.2 Raceway and Nipple Calculations.....198

5.3 Existing Raceway Calculations.....199

5.4 Tips for Raceway Calculations.....201

### PART B—OUTLET BOX FILL CALCULATIONS [314.16] .....201

5.5 Sizing Box—Conductors All the Same Size  
[Table 314.16(A)] .....201

5.6 Conductor Equivalents [314.16(B)] .....202

5.7 Sizing Box—Different Size Conductors  
[314.16(B)] .....204

### PART C—PULL BOXES, JUNCTION BOXES, AND CONDUIT BODIES .....206

5.8 Pull and Junction Box Size Calculations .....207

5.9 Depth of Box and Conduit Body Sizing  
[314.28(A)(2) Ex].....208

5.10 Junction and Pull Box Sizing Tips .....208

5.11 Pull Box Examples .....209

Conclusion .....210

## UNIT 6—CONDUCTOR SIZING AND PROTECTION CALCULATIONS.....237

Introduction .....237

### PART A—GENERAL CONDUCTOR REQUIREMENTS.....237

6.1 Conductor Insulation Property [Table 310.13] .....237

6.2 Allowable Conductor Ampacity [310.15] .....239

6.3 Conductor Sizing [110.6] .....240

6.4 Terminal Ratings [110.14(C)] .....240

6.5 Conductors in Parallel [310.4] .....242

6.6 Conductor Size—Voltage Drop [210.19(A)(1)  
FPN No. 4 and 215.2(A) FPN No. 2] .....244

6.7 Overcurrent Protection [Article 240] .....244

6.8 Overcurrent Protection of Conductors—  
General Requirements [240.4] .....246

6.9 Overcurrent Protection of Conductors—  
Specific Requirements.....247

6.10 Equipment Conductor Size and  
Protection Examples.....248

### PART B—CONDUCTOR AMPACITY CALCULATIONS.....249

6.11 Conductor Ampacity [310.10].....249

6.12 Ambient Temperature Ampacity Correction  
Factor [Table 310.16] .....250

6.13 Conductor Bundling Ampacity Adjustment  
Factor [Table 310.15(B)(2)(a)].....251

6.14 Ambient Temperature Correction and Conductor  
Bundling Adjustment Factors .....253

6.15 Current-Carrying Conductors.....254

6.16 Conductor Sizing Summary .....256

Conclusion.....257

## UNIT 7—MOTOR CALCULATIONS .....285

Introduction .....285

7.1 Single Motor Conductors [430.22(A)] .....285

7.2 Motor Overcurrent Protection .....286

7.3 Overload Protection [430.6(2) and 430.32(A)].....287

7.4 Branch-Circuit Short-Circuit Ground-Fault  
Protection [430.51] .....289

7.5 Feeder Conductor Size [430.24] .....291

7.6 Feeder Protection [430.61] .....291

7.7 Highest-Rated Motor [430.17] .....292

7.8 Motor Calculations Steps .....293

7.9 Motor Calculation Review .....293

7.10 Motor VA Calculations.....296

Conclusion.....297

## UNIT 8—VOLTAGE-DROP CALCULATIONS.....323

Introduction .....323

### PART A—CONDUCTOR RESISTANCE CALCULATIONS .....323

8.1 Conductor Resistance .....323

8.2 Conductor Resistance—Direct-Current Circuits  
[Chapter 9, Table 8].....325

8.3 Conductor Impedance—  
Alternating-Current Circuits.....326

8.4 Alternating-Current Impedance as Compared to  
Direct-Current Resistance .....326

8.5 Impedance [Chapter 9, Table 9] .....326

### PART B—VOLTAGE-DROP CALCULATIONS.....329

8.6 Voltage-Drop Considerations .....329

8.7 NEC Voltage-Drop Recommendations.....329

8.8 Determining Circuit Conductors' Voltage Drop.....330

8.9 Sizing Conductors to Prevent Excessive  
Voltage Drop.....332

8.10 Limiting Conductor Length to Minimize  
Voltage Drop.....333

8.11 Limiting Current to Limit Voltage Drop .....334

8.12 Extending Circuits.....335

Conclusion.....336



<b>UNIT 9—DWELLING UNIT CALCULATIONS</b> .....	365	<b>UNIT 11—COMMERCIAL CALCULATIONS</b> .....	455
Introduction .....	365	Introduction .....	455
<b>PART A—GENERAL REQUIREMENTS</b> .....	365	<b>PART A—GENERAL</b> .....	455
9.1 General Requirements .....	365	11.1 General Requirements .....	455
9.2 Voltages [220.5(A)] .....	365	11.2 Conductor Ampacity [Article 100].....	455
9.3 Fraction of an Ampere [220.5(B)].....	365	11.3 Conductor Overcurrent Protection [240.4].....	456
9.4 Small-Appliance Circuits [210.11(C)(1)] .....	366	11.4 Voltages [220.5(A)] .....	456
9.5 Cooking Equipment—Branch Circuit [Table 220.55, Note 4].....	367	11.5 Rounding an Ampere [220.5(B)].....	456
9.6 Laundry Receptacle(s) Circuit [210.11(C)(2)].....	369	11.6 Air-Conditioning Branch Circuit.....	457
9.7 Lighting and Receptacles .....	369	11.7 Dryers .....	458
<b>PART B—STANDARD METHOD— FEEDER/SERVICE LOAD CALCULATIONS</b> .....	371	11.8 Electric Heat .....	459
9.8 Dwelling Unit Feeder/Service Load Calculations (Article 220, Part III).....	371	11.9 Kitchen Equipment.....	460
9.9 Dwelling Unit Feeder/Service Calculations Examples .....	372	11.10 Laundry Equipment.....	461
<b>PART C—OPTIONAL METHOD— FEEDER/SERVICE LOAD CALCULATIONS</b> .....	376	11.11 Lighting—Demand Factors [Tables 220.12 and 220.42] .....	462
9.10 Dwelling Unit Optional Feeder/Service Calculations [220.82] .....	376	11.12 Lighting Without Demand Factors [215.2(A)(1), 230.42(A)(1), and Table 220.12].....	462
9.11 Dwelling Unit Optional Calculation Examples .....	377	11.13 Lighting-Miscellaneous.....	463
9.12 Neutral Calculations—General [220.61].....	378	11.14 Multioutlet Receptacle Assembly [220.14(H)] .....	463
Conclusion.....	380	11.15 Receptacle VA Load .....	464
<b>UNIT 10—MULTIFAMILY DWELLING CALCULATIONS</b> .....	411	11.16 Banks and Offices—General Lighting and Receptacles [220.14(K)].....	465
Introduction .....	411	11.17 Signs [220.14(F) and 600.5].....	467
10.1 Multifamily Dwelling Unit Calculations— General .....	411	<b>PART B—STANDARD METHOD— FEEDER/SERVICE LOAD CALCULATIONS</b> .....	467
<b>PART A—STANDARD METHOD— FEEDER/SERVICE LOAD CALCULATIONS</b> .....	413	11.18 Feeder/Service Load Calculation .....	467
10.2 Multifamily Dwelling Unit Calculation Examples—Standard Method.....	413	11.19 Neutral Calculations [220.61] .....	467
10.3 Multifamily Dwelling Unit Calculations— Standard Method .....	419	<b>PART C—EXAMPLES</b> .....	469
<b>PART B—OPTIONAL METHOD— FEEDER/SERVICE LOAD CALCULATIONS</b> .....	421	11.20 Bank (120/240V, single-phase) .....	469
10.4 Multifamily Dwelling Unit Calculations [220.84]—Optional Method.....	421	11.21 Marina [555.12].....	470
10.5 Multifamily—Optional Method Example 1 [220.84] .....	422	11.22 Mobile/Manufactured Home Park [550.31] .....	471
10.6 Multifamily—Optional Method Example 2 [220.84] .....	424	11.23 Office Building (277/480V, Three-phase).....	472
Conclusion.....	426	11.24 Recreational Vehicle Park [551.73].....	474
		11.25 Restaurant—Standard Load Calculation (120/208V, Three-phase) .....	474
		<b>PART D—OPTIONAL METHOD— FEEDER/SERVICE LOAD CALCULATIONS</b> .....	476
		11.26 New Restaurant—Optional Method [220.88] .....	476
		11.27 School—Optional Method [220.86].....	478
		<b>PART E—ELECTRIC WELDERS</b> .....	479
		11.28 Arc Welders .....	479
		11.29 Resistance Welders .....	480
		11.30 Light Industrial Calculation .....	481
		Conclusion.....	482

**UNIT 12—DELTA/DELTA AND DELTA/WYE TRANSFORMERS**.....511

Introduction .....511  
 Definitions .....511  
 12.1 Current Flow.....515

**PART A—DELTA/DELTA TRANSFORMERS** .....516

12.2 Delta Transformer Voltage.....516  
 12.3 Delta High-Leg.....516  
 12.4 Delta Line Currents .....517  
 12.5 Delta Phase Currents .....517  
 12.6 Delta Phase versus Line Current .....518  
 12.7 Delta Current Triangle.....519  
 12.8 Delta Transformer Balancing .....520  
 12.9 Delta Transformer Sizing .....521  
 12.10 Delta Panel Balancing .....521  
 12.11 Delta Panelboard and Conductor Sizing .....521  
 12.12 Delta Neutral Current .....522  
 12.13 Delta Maximum Unbalanced Load .....523  
 12.14 Delta/Delta Example .....523

**PART B—DELTA/WYE TRANSFORMERS**.....526

12.15 Wye Transformer Voltage .....526  
 12.16 Wye Voltage Triangle .....526  
 12.17 Wye Transformers Current .....526  
 12.18 Wye Line Current .....527  
 12.19 Wye Phase Current .....527  
 12.20 Wye Phase versus Line Current .....528  
 12.21 Wye Transformer Balancing.....529  
 12.22 Wye Transformer Sizing.....530  
 12.23 Wye Panel Balancing.....530  
 12.24 Wye Panelboard and Conductor Sizing.....531  
 12.25 Wye Neutral Current .....531  
 12.26 Wye Maximum Unbalanced Load.....532  
 12.27 Delta/Wye Example.....532  
 12.28 Delta versus Wye.....536  
 Conclusion.....536

**INDEX**.....567

