



Table of Contents

INTRODUCTION	xiii
Author's Comments.....	xiii
Exam Preparation.....	xiii
Difficult Concepts.....	xiv
Textbook Errors and Corrections.....	xv
Internet.....	xv

UNIT 1—ELECTRICIAN'S MATH AND BASIC ELECTRICAL FORMULAS..... 1

PART A—ELECTRICIAN'S MATH	1
1.1 Whole Numbers.....	1
1.2 Decimals	1
1.3 Fractions.....	1
1.4 Percentages	1
1.5 Multiplier.....	2
1.6 Percent Increase	2
1.7 Reciprocals.....	2
1.8 Squaring a Number	3
1.9 Parentheses	3
1.10 Square Root.....	4
1.11 Volume.....	4
1.12 Kilo.....	4
1.13 Rounding Off.....	5
1.14 Testing Your Answer for Reasonableness.....	6

PART B—BASIC ELECTRICAL FORMULAS	6
1.15 Electrical Circuit.....	6
1.16 Power Source	7
1.17 Conductance.....	8
1.18 Circuit Resistance	8
1.19 Ohm's Law.....	8
1.20 Ohm's Law and Alternating Current.....	8
1.21 Ohm's Law Formula Circle	8
1.22 PIE Formula Circle.....	10
1.23 Formula Wheel	11
1.24 Using the Formula Wheel	11
1.25 Power Losses of Conductors.....	12
1.26 Cost of Power	13
1.27 Power Changes with the Square of the Voltage.....	14

UNIT 2—ELECTRICAL CIRCUITS	15
PART A—SERIES CIRCUITS	15
Introduction	15
2.1 Practical Uses of the Series Circuit	15
2.2 Understanding Series Calculations	16
2.3 Series Circuit Calculations	17
2.4 Power Calculations	18
2.5 Variations	19
2.6 Series Circuit Notes	19
2.7 Series-Connected Power Supplies	19
PART B—PARALLEL CIRCUITS	19
Introduction	19
2.8 Practical Uses of the Parallel Circuit	20
2.9 Understanding Parallel Calculations	20
2.10 Circuit Resistance	20
2.11 Parallel Circuit Notes	22
2.12 Parallel-Connected Power Supplies	22
PART C—SERIES-PARALLEL CIRCUITS	22
Introduction	22
2.13 Review of Series and Parallel Circuits	23
2.14 Working With Series-Parallel Circuits	24
2.15 Voltage	26
PART D—MULTIWIRE BRANCH CIRCUITS	26
Introduction	26
2.16 Neutral Conductor	26
2.17 Grounded Conductor	27
2.18 Current Flow on the Grounded (Neutral) Conductor	27
2.19 Balanced Systems	27
2.20 Unbalanced Current	28
2.21 Multiwire Branch Circuits	29
2.22 Dangers of Multiwire Branch Circuits	29
2.23 NEC Requirements	31
UNIT 3—UNDERSTANDING ALTERNATING CURRENT	33
PART A—UNDERSTANDING ALTERNATING CURRENT	33
Introduction	33
3.1 Current Flow	33
3.2 Why Alternating Current is Used	33
3.3 How Alternating Current is Produced	33
3.4 AC Generator	34
3.5 Waveform	35

3.6	Sine Wave.....	35
3.7	Frequency	36
3.8	Phase.....	37
3.9	Degrees	37
3.10	Lead or Lag	37
3.11	Values of Alternating Current	37

PART B—CAPACITANCE..... 39

Introduction.....	39
3.12 Charged Capacitor.....	39
3.13 Electrical Field.....	39
3.14 Discharging a Capacitor	39
3.15 Determining Capacitance	40
3.16 Uses of Capacitors.....	40
3.17 Phase Relationship.....	41

PART C—INDUCTION 41

Introduction.....	41
3.18 Self-Induction	42
3.19 Induced Voltage and Applied Current	42
3.20 Conductor AC Resistance.....	43
3.21 Impedance	43
3.22 Conductor Shape	43
3.23 Magnetic Cores.....	44
3.24 Self-Induced and Applied Voltage.....	45
3.25 Current Flow	45
3.26 Phase Relationship.....	45
3.27 Uses of Induction	46

PART D—POWER FACTOR..... 47

Introduction.....	47
3.28 Apparent Power (Volt-Amperes).....	47
3.29 True Power (Watts)	47
3.30 Power Factor.....	48
3.31 Unity Power Factor	49
3.32 Power Factor Formulas.....	50
3.33 Cost of True Power.....	51
3.34 Effects of Low Power Factor	52

PART E—EFFICIENCY..... 52

Introduction.....	52
3.35 Efficiency Formulas	52

UNIT 4—MOTORS AND TRANSFORMERS..... 55

PART A—MOTORS 55

Introduction.....	55
4.1 Motor Principles.....	55
4.2 Dual-Voltage AC Motors.....	55

4.3	Motor Horsepower Rating.....	56
4.4	Motor Current Ratings.....	57
4.5	Calculating Motor FLA.....	58
4.6	Motor-Starting Current	59
4.7	Motor-Running Current	59
4.8	Motor Locked-Rotor Current (LRC).....	59
4.9	Motor Overload Protection	60
4.10	Direct-Current Motor Principles	61
4.11	Direct-Current Motor Types.....	61
4.12	Reversing the Rotation of a DC Motor	62
4.13	AC Induction Motor	62
4.14	Alternating-Current Motor Types.....	63
4.15	Reversing the Rotation of an AC Motor	65

PART B—TRANSFORMERS

Introduction.....	65
4.16 Transformer Basics	65
4.17 Secondary Induced Voltage.....	66
4.18 Transformer Turns Ratio	66
4.19 Autotransformers.....	69
4.20 Power Losses.....	70
4.21 Harmonic Current	71
4.22 Efficiency	71
4.23 Transformer kVA Rating.....	71
4.24 Current Rating.....	72

UNIT 5—RACEWAY AND BOX CALCULATIONS

PART A—RACEWAY FILL

5.1 Understanding the <i>NEC</i> , Chapter 9 Tables.....	75
5.2 Raceway and Nipple Calculations.....	78
5.3 Existing Raceway Calculations	80
5.4 Tips for Raceway Calculations.....	81

PART B—OUTLET BOX FILL CALCULATIONS

5.5 Sizing Box—Conductors All the Same Size	82
5.6 Conductor Equivalents	83
5.7 Sizing Box—Different Size Conductors	88

PART C—PULL BOXES, JUNCTION BOXES, AND CONDUIT BODIES

5.8 Pull and Junction Box Size Calculations.....	89
5.9 Depth of Box and Conduit Body Sizing	93
5.10 Junction and Pull Box Sizing Tips	93
5.11 Pull Box Examples.....	94

UNIT 6—CONDUCTOR SIZING AND PROTECTION CALCULATIONS 95

PART A—GENERAL CONDUCTOR REQUIREMENTS 95

6.1	Conductor Insulation Property	95
6.2	Allowable Conductor Ampacity	95
6.3	Conductor Sizing	97
6.4	Terminal Ratings	97
6.5	Conductors in Parallel	101
6.6	Conductor Size—Voltage Drop	101
6.7	Overcurrent Protection	101
6.8	Overcurrent Protection of Conductors— General Requirements	103
6.9	Overcurrent Protection of Conductors— Specific Requirements.....	105
6.10	Equipment Conductor Size and Protection Examples	106

PART B—CONDUCTOR AMPACITY CALCULATIONS 109

6.11	Conductor Ampacity	109
6.12	Ambient Temperature Ampacity Correction Factor	109
6.13	Conductor Bundling Ampacity Adjustment Factor	112
6.14	Ambient Temperature Correction and Conductor Bundling Adjustment Factors	113
6.15	Current-Carrying Conductors	115
6.16	Conductor Sizing Summary.....	119

UNIT 7—MOTOR CALCULATIONS 121

7.1	Single Motor Conductors	121
7.2	Motor Overcurrent Protection.....	122
7.3	Overload Protection	124
7.4	Branch-Circuit Short-Circuit Ground-Fault Protection	125
7.5	Feeder Conductor Size.....	128
7.6	Feeder Protection.....	129
7.7	Highest Rated Motor	131
7.8	Motor Calculations Steps	131
7.9	Motor Calculation Review.....	133
7.10	Motor VA Calculations.....	139

UNIT 8—VOLTAGE-DROP CALCULATIONS 141

PART A—CONDUCTOR RESISTANCE CALCULATIONS 141

8.1	Conductor Resistance	141
8.2	Conductor Resistance—Direct-Current Circuits ..	142

8.3	Conductor Impedance—Alternating-Current Circuits	143
8.4	Alternating-Current Impedance as Compared to Direct-Current Resistance	144
8.5	Impedance	146
PART B—VOLTAGE-DROP CALCULATIONS		148
8.6	Voltage-Drop Considerations.....	148
8.7	NEC Voltage-Drop Recommendations	149
8.8	Determining Circuit Conductors' Voltage Drop	150
8.9	Sizing Conductors to Prevent Excessive Voltage Drop.....	154
8.10	Limiting Conductor Length to Minimize Voltage Drop.....	157
8.11	Limiting Current to Limit Voltage Drop	157
8.12	Extending Circuits	157

UNIT 9—DWELLING UNIT CALCULATIONS ... 161

PART A—GENERAL REQUIREMENTS		161
9.1	General Requirements	161
9.2	Voltages	161
9.3	Fraction of an Ampere	161
9.4	Small-Appliance Circuits	161
9.5	Cooking Equipment—Branch Circuit	162
9.6	Laundry Receptacle(s) Circuit	167
9.7	Lighting and Receptacles	168

PART B—STANDARD METHOD—FEEDER/SERVICE LOAD CALCULATIONS..... 169

9.8	Dwelling Unit Feeder/Service Load Calculations	169
9.9	Dwelling Unit Feeder/Service Calculations Examples	171

PART C—OPTIONAL METHOD—FEEDER/SERVICE LOAD CALCULATIONS..... 176

9.10	Dwelling Unit Optional Feeder/Service Calculations	176
9.11	Dwelling Unit Optional Calculation Example	178
9.12	Neutral Calculations—General	179

UNIT 10—MULTIFAMILY DWELLING CALCULATIONS 181

10.1	Multifamily Dwelling Unit Calculations— General	181
------	--	-----

PART A—STANDARD METHOD-FEEDER/SERVICE LOAD CALCULATIONS	184
10.2 Multifamily Dwelling Unit Calculations— Standard Method	184
PART B—OPTIONAL METHOD-FEEDER/SERVICE LOAD CALCULATIONS	186
10.3 Multifamily Dwelling Unit Calculations — Optional Method	186
10.4 Multifamily—Optional Method Example	187
UNIT 11—COMMERCIAL CALCULATIONS	191
PART A—GENERAL	191
11.1 General Requirements	191
11.2 Conductor Ampacity	191
11.3 Voltages	192
11.4 Rounding an Ampere	192
11.5 Air-Conditioning Branch Circuit	192
11.6 Dryers	193
11.7 Electric Heat	194
11.8 Kitchen Equipment	194
11.9 Laundry Equipment	196
11.10 Lighting—Demand Factors	197
11.11 Lighting Without Demand Factors	197
11.12 Lighting-Miscellaneous	198
11.13 Multioutlet Receptacle Assembly	198
11.14 Receptacle VA Load	198
11.15 Banks and Offices—General Lighting and Receptacles	200
11.16 Signs	201
PART B—STANDARD METHOD—FEEDER/SERVICE LOAD CALCULATIONS	201
11.17 Feeder/Service Load Calculation	201
11.18 Neutral Calculations	202
PART C—EXAMPLES	204
11.19 Bank (120/240V, Single-Phase)	204
11.20 Marina	206
11.21 Mobile/Manufactured Home Park	207
11.22 Office Building (277/480V, Three-Phase)	208
11.23 Recreational Vehicle Park	211
11.24 Restaurant—Standard Load Calculation (120/208V, Three-Phase)	212
PART D—OPTIONAL METHOD—FEEDER/SERVICE LOAD CALCULATIONS	215

11.25	New Restaurant—Optional Method	215
11.26	School—Optional Method	218
PART E—ELECTRIC WELDERS		220
11.27	Arc Welders	220
11.28	Resistance Welders.....	222

UNIT 12—DELTA/DELTA AND DELTA/WYE TRANSFORMERS

Definitions.....	225
12.1 Current Flow	233

PART A—DELTA/DELTA TRANSFORMERS

12.2	Delta Transformer Voltage	235
12.3	Delta High-Leg.....	235
12.4	Delta Line Currents.....	236
12.5	Delta Phase Currents.....	237
12.6	Delta Phase versus Line Current	238
12.7	Delta Current Triangle	240
12.8	Delta Transformer Balancing	240
12.9	Delta Transformer Sizing.....	241
12.10	Delta Panel Balancing	242
12.11	Delta Panelboard and Conductor Sizing	242
12.12	Delta Neutral Current	242
12.13	Delta Maximum Unbalanced Load.....	242

PART B—DELTA/WYE TRANSFORMERS.....

12.14	Wye Transformer Voltage	242
12.15	Wye Voltage Triangle.....	242
12.16	Wye Transformer Current.....	243
12.17	Wye Line Current	243
12.18	Wye Phase Current	245
12.19	Wye Transformer Balancing	246
12.20	Wye Transformer Sizing.....	247
12.21	Wye Panel Balancing	247
12.22	Wye Panelboard and Conductor Sizing.....	247
12.23	Wye Neutral Current	247
12.24	Wye Maximum Unbalanced Load.....	248
12.25	Delta versus Wye	248

COMMERCIAL WIRE AND RACEWAY CHART

.....	250
-------	-----

FORMULAS

.....	252
-------	-----