

# TABLE OF CONTENTS

**Introduction**.....xv

**About the Mike Holt Enterprises Team**..... xviii

## **CHAPTER 1—ELECTRICAL THEORY** ..... 1

### **Unit 1—Electrician’s Math and Basic Electrical Formulas**..... 1

#### **Part A—Electrician’s Math** ..... 1

1.1	Whole Numbers	1
1.2	Decimals	1
1.3	Fractions	1
1.4	Percentages	2
1.5	Multiplier	2
1.6	Percent Increase	3
1.7	Reciprocals	3
1.8	Squaring a Number	4
1.9	Parentheses	4
1.10	Square Root	4
1.11	Volume	5
1.12	Kilo	5
1.13	Rounding Off	6
1.14	Testing Your Answer for Reasonableness	7

#### **Part B—Basic Electrical Formulas** ..... 8

1.15	Electrical Circuit	8
1.16	Power Source	8
1.17	Conductance	9
1.18	Circuit Resistance	9

1.19	Ohm's Law .....	10
1.20	Ohm's Law and Alternating Current .....	10
1.21	Ohm's Law Formula Circle .....	11
1.22	PIE Formula Circle.....	12
1.23	Formula Wheel.....	13
1.24	Using the Formula Wheel .....	13
1.25	Power Losses of Conductors.....	14
1.26	Cost of Power .....	14
1.27	Power Changes with the Square of the Voltage .....	16

## **Unit 2—Electrical Circuits** ..... 17

### **Part A—Series Circuits** ..... 17

Introduction .....		17
2.1	Practical Uses of the Series Circuit.....	17
2.2	Understanding Series Calculations.....	18
2.3	Series Circuit Calculations .....	20
2.4	Power Calculations .....	20
2.5	Variations.....	20
2.6	Series Circuit Notes .....	21
2.7	Series-Connected Power Supplies .....	21

### **Part B—Parallel Circuits** ..... 22

Introduction .....		22
2.8	Practical Uses of the Parallel Circuit.....	22
2.9	Understanding Parallel Calculations .....	22
2.10	Circuit Resistance .....	23
2.11	Parallel Circuit Notes.....	25
2.12	Parallel-Connected Power Supplies.....	25

### **Part C—Series-Parallel Circuits** ..... 26

Introduction .....		26
2.13	Review of Series and Parallel Circuits .....	26
2.14	Working With Series-Parallel Circuits .....	27
2.15	Voltage .....	30

<b>Part D—Multiwire Branch Circuits</b> .....	30
Introduction .....	30
2.16 Neutral Conductor.....	30
2.17 Grounded Conductor .....	30
2.18 Current Flow on the Neutral Conductor .....	31
2.19 Balanced Systems .....	33
2.20 Unbalanced Current .....	33
2.21 Multiwire Branch Circuits.....	34
2.22 Dangers of Multiwire Branch Circuits.....	34
2.23 <b>NEC</b> Requirements .....	37
<b>Unit 3—Understanding Alternating Current</b> .....	39
<b>Part A—Understanding Alternating Current</b> .....	39
Introduction .....	39
3.1 Current Flow .....	39
3.2 Why Alternating Current Is Used.....	39
3.3 How Alternating Current Is Produced .....	39
3.4 Alternating-Current Generator.....	40
3.5 Waveform .....	41
3.6 Sine Wave.....	42
3.7 Frequency.....	43
3.8 Phase .....	43
3.9 Degrees.....	44
3.10 Lead or Lag .....	45
3.11 Values of Alternating Current.....	46
<b>Part B—Capacitance</b> .....	47
Introduction .....	47
3.12 Charged Capacitor .....	48
3.13 Electrical Field .....	48
3.14 Discharging a Capacitor.....	48
3.15 Determining Capacitance.....	48
3.16 Uses of Capacitors .....	49
3.17 Phase Relationship .....	50

<b>Part C—Induction</b> .....	51
Introduction .....	51
3.18 Self-Induction .....	51
3.19 Induced Voltage and Applied Current.....	52
3.20 Conductor Alternating-Current Resistance .....	52
3.21 Conductor Shape .....	53
3.22 Magnetic Cores.....	54
3.23 Self-Induced and Applied Voltage.....	55
3.24 Inductive Reactance.....	55
3.25 Phase Relationship .....	55
3.26 Uses of Induction .....	55
<b>Part D—Power Factor</b> .....	57
Introduction .....	57
3.27 Apparent Power (Volt-Amperes).....	57
3.28 True Power (Watts).....	58
3.29 Power Factor .....	58
3.30 Unity Power Factor.....	58
3.31 Power Factor Formulas .....	60
3.32 Cost of True Power.....	61
3.33 Effects of Power Factor .....	62
<b>Part E—Efficiency</b> .....	62
Introduction .....	62
3.34 Efficiency Formulas.....	62
<b>Unit 4—Motors and Transformers</b> .....	65
<b>Part A—Motor Basics</b> .....	65
Introduction .....	65
4.1 Motor Principles.....	65
4.2 Dual-Voltage Alternating-Current Motors .....	65
4.3 Motor Horsepower Ratings .....	66
4.4 Motor Current Ratings.....	67
4.5 Calculating Motor FLA.....	68

4.6	Motor-Starting Current.....	70
4.7	Motor-Running Current .....	70
4.8	Motor Locked-Rotor Current (LRC).....	70
4.9	Motor Overload Protection .....	71
4.10	Direct-Current Motor Principles.....	72
4.11	Direct-Current Motor Types.....	73
4.12	Reversing the Rotation of a Direct-Current Motor.....	73
4.13	Alternating-Current Induction Motor.....	74
4.14	Alternating-Current Motor Types .....	75
4.15	Reversing the Rotation of an Alternating-Current Motor .....	76
<b>Part B—Transformers .....</b>		<b>77</b>
Introduction .....		77
4.16	Transformer Basics.....	77
4.17	Secondary Induced Voltage.....	77
4.18	Efficiency.....	79
4.19	Transformer Turns Ratio.....	79
4.20	Power Losses .....	81
4.21	Transformer kVA Rating .....	82
4.22	Current Flow .....	83
4.23	Current Rating .....	84
4.24	Autotransformers.....	85
<b>CHAPTER 2—NEC CALCULATIONS .....</b>		<b>87</b>
<b>Unit 5—Raceway and Box Calculations .....</b>		<b>87</b>
<b>Part A—Raceway Sizing .....</b>		<b>87</b>
Introduction .....		87
5.1	Insulated Conductors and Fixture Wires Dimensions— Chapter 9, Tables 5 and 8 .....	87
5.2	Raceway Properties .....	88
5.3	Raceway Sizing .....	91
5.4	Sizing Raceways Using Annex C .....	92
5.5	Sizing Wireways.....	93
5.6	Tips for Raceway Calculations .....	94

<b>Part B—Outlet Box Fill</b> .....	94
Introduction .....	94
5.7 Box Volume Calculations [314.16].....	95
5.8 Sizing Box—Conductors All the Same Size .....	95
5.9 Box Fill Calculations [314.16(B)] .....	96
5.10 Outlet Box Sizing.....	99
<b>Part C—Pull Boxes, Junction Boxes, and Conduit Bodies</b> .....	101
Introduction .....	101
5.11 Pull/Junction Box Sizing Requirements .....	101
5.12 Pull/Junction Box Sizing Tips .....	102
5.13 Pull Box Examples .....	103
<b>Unit 6—Conductor Sizing and Protection Calculations</b> .....	107
<b>Part A—Conductor Requirements</b> .....	107
6.1 Conductor Insulation [310.104(A)].....	107
6.2 Conductor Sizes.....	109
6.3 Smallest Conductor Size [310.106].....	109
6.4 Conductor Size—Equipment Terminal Rating [110.14(C)] .....	110
6.5 Overcurrent Protection [Article 240].....	114
<b>Part B—Conductor Ampacity</b> .....	117
Introduction .....	117
6.6 Conductor Heating— $I^2R$ .....	117
6.7 Limiting Excessive Temperature.....	118
6.8 Conductor Ampacity.....	119
6.9 Ambient Temperature Correction [310.15(B)(2)(a)] .....	119
6.10 Rooftop Temperature Adder [310.15(B)(3)(c)] .....	122
6.11 Ampacity Adjustment [310.15(B)(3)(a)].....	123
6.12 Combining Ambient Temperature and Conductor Bundling Adjustments .....	126
6.13 Current-Carrying Conductors .....	127
6.14 Wireway—Conductor Ampacity Adjustment.....	130
6.15 Conductor Ampacity Summary.....	130

6.16	Conductor Sizing.....	131
6.17	Feeder Tap Rules .....	134
<b>Unit 7—Voltage-Drop Calculations.....</b>		<b>145</b>
<b>Part A—Conductor Resistance Calculations .....</b>		<b>145</b>
7.1	Conductor Size .....	145
7.2	Conductor Resistance .....	146
7.3	Alternating-Current Conductor Resistance .....	149
7.4	Alternating-Current Resistance [Chapter 9, Table 9].....	150
7.5	AC versus DC Resistance.....	152
<b>Part B—Voltage-Drop Considerations .....</b>		<b>153</b>
Introduction .....		153
7.6	<i>NEC</i> Voltage-Drop Recommendations .....	154
7.7	Determining Circuit Conductors' Voltage Drop— Ohm's Law Method.....	155
7.8	Determining Circuit Conductors' Voltage Drop— Formula Method .....	156
7.9	Sizing Conductors to Account for Voltage Drop.....	159
7.10	Limiting Conductor Length to Minimize Voltage Drop .....	160
7.11	Limiting Current to Limit Voltage Drop.....	162
<b>Unit 8—Motor and Air-Conditioning Calculations .....</b>		<b>165</b>
<b>Part A—Motor Calculations.....</b>		<b>165</b>
8.1	Scope of Article 430.....	165
8.2	Motor Full Load Current (FLC) [430.6(A)(1)].....	166
8.3	Motor Nameplate Full Load Amperes (FLA) [430.6(A)(2)] .....	168
8.4	Branch-Circuit Conductor Sizing [430.22] .....	169
8.5	Feeder Conductor Sizing [430.24].....	171
8.6	Overcurrent Protection.....	172
8.7	Overload Protection Sizing .....	174
8.8	Branch-Circuit Short-Circuit and Ground-Fault Protection.....	179

8.9	Branch Circuit Summary .....	183
8.10	Combined Branch Circuit Overcurrent Protection [430.55] .....	184
8.11	Feeder Short-Circuit and Ground-Fault Protection [430.62].....	184
8.12	Motor VA Calculations .....	185
8.13	Adjustable Speed Drives .....	187
8.14	Fire Pump Motor Circuits .....	188
<b>Part B—Air-Conditioning Calculations .....</b>		<b>189</b>
8.15	Scope of Article 440.....	189
8.16	Multimotor Equipment [440.4(B)] .....	190
8.17	Motor-Compressor and Other Motors—Short-Circuit and Ground-Fault Protection [440.22(B)(1)].....	191
8.18	Motor-Compressor and Other Motors—Conductor Size [440.33].....	191
<b>Unit 9—Dwelling Unit Calculations .....</b>		<b>193</b>
<b>Part A—Standard Method Load Calculations [Article 220, Part III] .....</b>		<b>193</b>
Introduction .....		193
9.1	General Lighting and General-Use Receptacle Demand Load [220.42] .....	195
9.2	Appliance Demand Load [220.53].....	196
9.3	Dryer Demand Load [220.54] .....	197
9.4	Cooking Equipment Demand Load [220.55].....	197
9.5	Air-Conditioning versus Heat Demand Load [220.60].....	199
9.6	Service Conductor Sizing [310.15(B)(7)].....	200
9.7	Standard Method Load Calculations Example .....	202
<b>Part B—Optional Method Load Calculations [Article 220, Part IV] .....</b>		<b>204</b>
Introduction .....		204
9.8	Dwelling Unit Optional Load Calculation [220.82].....	204
9.9	Dwelling Unit Optional Load Calculation [220.82] Example...	206
9.10	Existing Dwelling Unit Optional Load Calculation [220.83]...	207



<b>CHAPTER 3—ADVANCED <i>NEC</i> CALCULATIONS</b> .....	209
<b>Unit 10—Multifamily Dwelling Calculations</b> .....	209
Introduction .....	209
<b>Part A—Standard Method Load Calculations</b>	
<b>[Article 220, Part III]</b> .....	209
10.1 General Lighting and General-Use Receptacle Demand Load [220.42] .....	211
10.2 Appliance Demand Load [220.53] .....	212
10.3 Dryer Demand Load [220.54] .....	213
10.4 Cooking Equipment Demand Load [220.55] .....	214
10.5 Air-Conditioning versus Heat Demand Load [220.60] .....	216
10.6 Service Conductor Sizing [310.15(B)(16)] .....	216
10.7 Multifamily Dwelling Calculations—Standard Method Example .....	217
<b>Part B—Optional Method Load Calculations</b>	
<b>[Article 220, Part IV]</b> .....	220
Introduction .....	220
10.8 Multifamily Dwelling Optional Load Calculations [220.84] .....	220
10.9 Multifamily Dwelling Optional Method Example [220.84] .....	221
10.10 Two-Family Dwelling Units [220.85] .....	223
<b>Unit 11—Commercial Calculations</b> .....	229
<b>Part A—General</b> .....	229
11.1 Lighting—Demand Factors [Tables 220.12 and 220.42] .....	229
11.2 Lighting Load 100% Demand .....	231
11.3 Sign Circuit [220.14(F) and 600.5] .....	231
11.4 Show-Window Lighting [220.14(G)] .....	232
11.5 Multioutlet Receptacle Assembly [220.14(H)] .....	232
11.6 Receptacle Load [220.14(I) and 220.44] .....	233
11.7 Banks and Offices—Receptacle Demand Load [220.14(K)] .....	235

<b>Unit 12—Transformer Calculations</b> .....	239
Introduction .....	239
<b>Part A—General</b> .....	240
12.1 Transformer Basics .....	240
12.2 Delta-Connected Transformers .....	241
12.3 Wye-Connected Transformers.....	243
12.4 Transformer kVA Rating .....	244
12.5 Line Currents .....	244
<b>Part B—NEC Requirements</b> .....	246
12.6 Transformer Overcurrent Protection .....	246
12.7 Primary Conductor Sizing.....	248
12.8 Secondary Conductor Sizing .....	249
<b>ANNEX A—COMMERCIAL/INDUSTRIAL WIRING, RACEWAY CHART, AND FORMULAS</b> .....	252
<b>INDEX</b> .....	257