

# TABLE OF CONTENTS

<b>About This Textbook</b> .....	ix	4.7 Secondary Distribution Voltage .....	23
<b>Additional Products to Help You Learn</b> .....	xii	4.8 Service Drop and Service Lateral.....	23
<b>Chapter 1—Practice Questions</b> .....25			
<b>CHAPTER 1—ELECTRICAL FUNDAMENTALS</b> .....1			
<b>Unit 1—Atomic Structure</b> .....	3	<b>CHAPTER 2—USES AND DANGERS OF ELECTRICITY</b> .....33	
1.1 Introduction .....	3	Unit 5—Uses of Electricity.....	35
1.2 Atomic Theory.....	3	5.1 Introduction .....	35
1.3 Electrostatic Field .....	4	5.2 Uses of Electricity.....	35
1.4 Atomic Charge of an Atom.....	5	5.3 Electrochemical Processes.....	35
1.5 Electrostatic Charge and Discharge.....	6	5.4 Electromagnetism.....	35
1.6 Lightning .....	7	5.5 Photoelectricity .....	36
1.7 Lightning Protection System.....	8	5.6 Electric Heating .....	37
5.7 Lighting .....	39		
<b>Unit 2—Electron Theory and Chemical Bonding</b> .....	9	<b>Unit 6—Dangers of Electricity</b> .....41	
2.1 Introduction .....	9	6.1 Introduction .....	41
2.2 Electron Orbitals.....	9	6.2 <i>National Electrical Code (NEC)</i> .....	41
2.3 Valence Electrons.....	9	6.3 Electrical Fire .....	41
2.4 Freeing Valence Electron(s) from an Atom.....	10	6.4 Electric Shock.....	42
2.5 Conductance .....	10	6.5 Electric Arc Flash and Arc Blast .....	43
2.6 Insulators .....	12	6.6 Arc Flash Incident Energy .....	44
2.7 Semiconductors.....	12	6.7 Electrically Safe Work Condition .....	45
2.8 Chemical Bonding .....	13	6.8 Personal Protective Equipment .....	46
<b>Chapter 2—Practice Questions</b> .....49			
<b>CHAPTER 3—MAGNETISM AND ELECTROMAGNETISM</b> .....55			
<b>Unit 3—Electrical Circuits and Power Sources</b> .....	15	<b>Unit 7—Basics of Magnetism</b> .....	57
3.1 Introduction .....	15	7.1 Introduction .....	57
3.2 The Electrical Circuit.....	15	7.2 The Natural Magnet .....	57
3.3 Electric Current Flow (Electricity).....	15	7.3 Magnetic Polarities .....	57
3.4 Electrical Power Sources .....	16	7.4 Theory of Magnetism.....	58
7.5 Permanent and Temporary Magnets .....	58		
7.6 Magnetizing and Demagnetizing Magnets.....	58		
<b>Unit 4—The Electrical System</b> .....	21		
4.1 Introduction .....	21		
4.2 Source of Electrical Generation.....	21		
4.3 Step-Up Transmission Voltage.....	21		
4.4 High-Voltage Transmission Lines.....	22		
4.5 Primary Distribution Voltage .....	22		
4.6 Primary Distribution Wires .....	22		

## Table of Contents |

---

7.7	Magnetic Lines of Force .....	59
7.8	Law of Attraction and Repulsion of Magnets.....	59

### **Unit 8—Electromagnetism** ..... 61

8.1	Introduction .....	61
8.2	Electromagnetism in a Wire.....	61
8.3	Electromagnet Field Interaction .....	62
8.4	Electromagnetic Field Interaction of Wire Loops.....	62
8.5	Electromagnetic Core .....	63

### **Unit 9—Uses of Electromagnetism** ..... 65

9.1	Introduction .....	65
9.2	Motors .....	65
9.3	Generators .....	66
9.4	Relays.....	66
9.5	Transformers .....	66

### **Chapter 3—Practice Questions** ..... 67

## **CHAPTER 4—MATHEMATICS** ..... 71

<b>Unit 10—Basic Math</b> .....	73	
10.1	Introduction .....	73
10.2	Whole Numbers.....	73
10.3	Fractional Numbers .....	73
10.4	Decimal Numbers.....	73
10.5	Percentages.....	74
10.6	Parentheses.....	75
10.7	Squaring a Number.....	75
10.8	Square Root.....	75
10.9	Kilo .....	76
10.10	Rounding .....	76
10.11	Surface Area of a Rectangle or Square .....	76
10.12	Surface Area of a Circle.....	77
10.13	Volume .....	79
10.14	Reciprocal.....	79
10.15	Testing Your Answer .....	79

### **Unit 11—Trigonometry** ..... 81

11.1	Introduction .....	81
11.2	Triangles.....	81
11.3	Right Triangle .....	81
11.4	Pythagorean Theorem.....	82
11.5	Practical Use of Trigonometry .....	83

### **Chapter 4—Practice Questions** ..... 85

## **CHAPTER 5—OHM'S LAW AND WATT'S LAW** ..... 91

### **Unit 12—Ohm's Law** ..... 93

12.1	Introduction .....	93
12.2	The Electrical Circuit.....	93
12.3	Electromotive Force (Pressure).....	93
12.4	Circuit Resistance .....	94
12.5	Circuit Intensity .....	95
12.6	Ohm's Law .....	95
12.7	Ohm's Law Formula Circle .....	96

### **Unit 13—Watt's Law** ..... 99

13.1	Introduction .....	99
13.2	Watt's Law .....	99
13.3	Power Formula Circle.....	100
13.4	Power Changes with the Square of the Voltage.....	101

### **Chapter 5—Practice Questions** ..... 103

## **CHAPTER 6—ELECTRICAL CIRCUIT TYPES** ..... 107

### **Unit 14—Series Circuits** ..... 109

14.1	Introduction .....	109
14.2	Series Circuits.....	109
14.3	Understanding Series Circuits .....	109
14.4	Series Circuit Summary.....	113
14.5	Series-Connected Power Supplies .....	113
14.6	Applications of Series Circuits.....	114

### **Unit 15—Parallel Circuits** ..... 117

15.1	Introduction .....	117
15.2	Understanding Parallel Circuits .....	117
15.3	Parallel Circuit Resistance Calculations .....	119
15.4	Parallel Circuit Summary.....	122
15.5	Parallel-Connected Power Supplies .....	122
15.6	Practical Uses of Parallel Circuits.....	123

### **Unit 16—Series-Parallel Circuits** ..... 125

16.1	Introduction .....	125
16.2	Understanding Series-Parallel Circuits .....	125
16.3	Calculating Resistance in Series-Parallel Circuits .....	126

### **Chapter 6—Practice Questions** ..... 129

<b>CHAPTER 7—ALTERNATING CURRENT .....</b>	137	<b>CHAPTER 8—MOTORS, GENERATORS, RELAYS, AND TRANSFORMERS .....</b>	177
<b>Unit 17—Alternating Current Fundamentals .....</b>	139	<b>Unit 21—Motors .....</b>	179
17.1 Introduction .....	139	21.1 Introduction .....	179
17.2 How Alternating Current is Produced .....	139	21.2 Alternating-Current Motor Principles .....	179
17.3 Waveforms .....	140	21.3 Motor Horsepower Rating .....	180
17.4 Frequency .....	143	21.4 Motor Amperes .....	181
17.5 In-Phase Waveforms .....	143	21.5 Motor Nameplate Amperes .....	182
17.6 Out-of-Phase Waveforms .....	143	21.6 Dual-Voltage Motors .....	184
17.7 Alternating-Current Waveform Values .....	144	21.7 Reversing the Rotation of Alternating-Current Motors .....	185
<b>Unit 18—Inductance .....</b>	147	21.8 Alternating-Current Motor Types .....	186
18.1 Introduction .....	147	<b>Unit 22—Generators .....</b>	187
18.2 How Inductance Works .....	147	22.1 Introduction .....	187
18.3 Self-Inductance .....	147	22.2 Generator Prime Mover .....	187
18.4 Mutual Inductance .....	148	22.3 Alternating-Current Generators .....	187
18.5 Inductive Reactance .....	149	22.4 Generator Output Current .....	188
18.6 Uses of Induction .....	150	22.5 Single-Phase and Three-Phase Generator Voltages .....	189
<b>Unit 19—Capacitance .....</b>	151	22.6 Electrical Industry Voltages .....	189
19.1 Introduction .....	151	<b>Unit 23—Relays .....</b>	191
19.2 Capacitance in Capacitors .....	151	23.1 Introduction .....	191
19.3 Capacitor Charge and Discharge .....	152	23.2 How Relays Operate .....	191
19.4 Capacitive Reactance .....	152	23.3 Relay Contacts .....	192
19.5 Uses of Capacitors .....	153	<b>Unit 24—Transformers .....</b>	193
<b>Unit 20—True Power, Power Factor, and Apparent Power .....</b>	155	24.1 Introduction .....	193
20.1 Introduction .....	155	24.2 Types of Transformers .....	193
20.2 True Power .....	155	24.3 Primary versus Secondary .....	193
20.3 Power Losses of Wires .....	156	24.4 Transformer Mutual Induction .....	194
20.4 Power Losses at Terminals .....	156	24.5 Secondary Induced Voltage .....	194
20.5 Equipment Efficiency .....	157	24.6 Transformer Turns Ratios .....	194
20.6 Cost of Power .....	158	24.7 Isolation Transformer (1:1) .....	196
20.7 Power Factor .....	159	24.8 Autotransformer .....	197
20.8 Apparent Power .....	160	24.9 Transformer kVA Rating .....	197
20.9 Apparent Power versus True Power .....	161	24.10 Transformer Current Flow .....	197
20.10 Effects of Power Factor on Circuits .....	162	24.11 Transformer Current Rating .....	197
<b>Chapter 7—Practice Questions .....</b>	165	24.12 Transformer Configurations .....	200
<b>Chapter 8—Practice Questions .....</b>	205	24.13 Delta/Wye Transformers .....	201
		24.14 Delta/Delta (High-Leg) Transformer .....	203

<b>CHAPTER 9—PROTECTIVE DEVICES .....</b>	215	<b>Unit 28—Multiwire Circuits .....</b>	249
<b>Unit 25—Overcurrent Protection.....</b>	217	28.1 Introduction .....	249
25.1 Introduction .....	217	28.2 Neutral Wire.....	249
25.2 Overcurrent Protection.....	217	28.3 Grounded Wire .....	250
25.3 Fuses .....	219	28.4 Current Flow on the Neutral Wire.....	250
25.4 Circuit Breakers.....	221	28.5 Multiwire Branch Circuits .....	251
25.5 Overcurrent Protective Devices, Time-Current Curves .....	222	28.6 Dangers of Multiwire Circuits .....	253
25.6 Available Short-Circuit Current .....	223	28.7 NEC Requirements .....	254
25.7 Overcurrent Protective Devices, Interrupting Rating.....	225		
25.8 Equipment Short-Circuit Current Rating (SCCR).....	225		
25.9 Coordination of Overcurrent Protective Devices.....	226		
<b>UNIT 26—GFCIs, GFPEs, AFCIs, AND SPDs .....</b>	229	<b>Unit 29—The Formula Wheel .....</b>	255
26.1 Introduction .....	229	29.1 Introduction .....	255
26.2 Ground-Fault Circuit Interrupters (GFCIs).....	229	29.2 Formula Wheel Quadrants .....	255
26.3 Special Purpose Ground-Fault Circuit Interrupters (SPGFCl)s).....	231	29.3 Using the Formula Wheel .....	256
26.4 Ground-Fault Protection of Equipment (GFPEs) .....	231		
26.5 Arc-Fault Circuit Interrupters (AFCIs).....	232		
26.6 Clearing Arcing Faults .....	232		
26.7 Surge Protective Devices (SPDs) .....	233		
26.8 How Surge Protective Device Functions.....	234		
<b>Chapter 9—Practice Questions.....</b>	235		
<b>CHAPTER 10—GENERAL KNOWLEDGE .....</b>	241	<b>FINAL EXAM .....</b>	267
<b>Unit 27—Wire Resistance and Voltage Drop .....</b>	243	<b>INDEX .....</b>	279
27.1 Introduction .....	243		
27.2 Wire Sizes .....	243		
27.3 Direct-Current Wire Resistance .....	243		
27.4 NEC Wire Direct-Current Resistance.....	244		
27.5 Alternating-Current Wire Resistance .....	245		
27.6 Alternating-Current Resistance versus Direct-Current Resistance .....	246		
27.7 Wire Voltage Drop—Ohm's Law Method .....	246		
		<b>About the Author .....</b>	283
		<b>About the Illustrator .....</b>	284
		<b>About the Mike Holt Team .....</b>	285