

Table of Contents

Introduction	x	1.24 Using the Formula Wheel	16
About This Textbook.....	xi	1.25 Power Losses of Conductors.....	17
Passing Your Exam.....	xiv	1.26 Cost of Power	17
How to Use the <i>National Electrical Code</i>	xviii	1.27 Power Changes with the Square of the Voltage	18
About the Author	xxi	Conclusion to Unit 1	20
About the Graphic Illustrator	xxii	Practice Questions for Unit 1	21
Mike Holt Enterprises Team.....	xxiii	Challenge Questions for Unit 1	27
CHAPTER 1—BASIC ELECTRICAL THEORY (Essential for Journeyman and Master's Licensing Exams)	1	UNIT 2—ELECTRICAL CIRCUITS	
UNIT 1—ELECTRICIAN'S MATH AND BASIC ELECTRICAL FORMULAS	3	Part A—Series Circuits	29
Part A—Electrician's Math	3	2.1 Practical Uses of the Series Circuit.....	29
1.1 Whole Numbers	3	2.2 Understanding Series Calculations.....	30
1.2 Decimals	3	2.3 Series Circuit Calculations	33
1.3 Fractions.....	3	2.4 Power Calculations	34
1.4 Percentages.....	4	2.5 Variations.....	34
1.5 Multiplier	4	2.6 Series Circuit Notes	34
1.6 Percent Increase	5	2.7 Series-Connected Power Supplies	34
1.7 Reciprocals.....	5	Part B—Parallel Circuits	34
1.8 Squaring a Number.....	6	2.8 Practical Uses of the Parallel Circuit	35
1.9 Parentheses.....	7	2.9 Understanding Parallel Calculations	37
1.10 Square Root.....	7	2.10 Circuit Resistance	38
1.11 Volume	8	2.11 Parallel Circuit Notes.....	40
1.12 Kilo	8	2.12 Parallel-Connected Power Supplies.....	40
1.13 Rounding Off.....	9	Part C—Series-Parallel Circuits	41
1.14 Testing Your Answer for Reasonableness.....	9	2.13 Review of Series and Parallel Circuits	41
Part B—Basic Electrical Formulas	10	2.14 Working With Series-Parallel Circuits.....	42
1.15 Electrical Circuit.....	10	2.15 Voltage	42
1.16 Power Source	10	Part D—Multiwire Branch Circuits	43
1.17 Conductance	11	2.16 Neutral Conductor	43
1.18 Circuit Resistance	11	2.17 Grounded Conductor	43
1.19 Ohm's Law	12	2.18 Current Flow on the Neutral Conductor	44
1.20 Ohm's Law and Alternating Current.....	12	2.19 Balanced Systems	45
1.21 Ohm's Law Formula Circle	12	2.20 Unbalanced Current	45
1.22 PIE Formula Circle.....	14	2.21 Multiwire Branch Circuits	46
1.23 Formula Wheel.....	15	2.22 Dangers of Multiwire Branch Circuits	48
		2.23 NEC Requirements	49
		Conclusion to Unit 2	49
		Practice Questions for Unit 2	51
		Challenge Questions for Unit 2	57

UNIT 3—UNDERSTANDING ALTERNATING CURRENT	61	UNIT 4—MOTORS AND TRANSFORMERS.....	95
Part A—Understanding Alternating Current.....	61	Part A—Motor Basics.....	95
3.1 Current Flow.....	61	4.1 Motor Principles.....	95
3.2 Why Alternating Current Is Used.....	62	4.2 Dual-Voltage Alternating-Current Motors.....	96
3.3 How Alternating Current Is Produced.....	62	4.3 Motor Horsepower Ratings.....	96
3.4 Alternating-Current Generator.....	62	4.4 Motor Current Ratings.....	97
3.5 Waveform	63	4.5 Calculating Motor FLA.....	97
3.6 Sine Wave.....	64	4.6 Motor-Starting Current.....	98
3.7 Frequency.....	64	4.7 Motor-Running Current	99
3.8 Phase	64	4.8 Motor Locked-Rotor Current (LRC)	99
3.9 Degrees.....	65	4.9 Motor Overload Protection.....	99
3.10 Lead or Lag	65	4.10 Direct-Current Motor Principles.....	100
3.11 Values of Alternating Current.....	65	4.11 Direct-Current Motor Types.....	100
Part B—Capacitance.....	66	4.12 Reversing the Rotation of a Direct-Current Motor	101
3.12 Charged Capacitor	67	4.13 Alternating-Current Induction Motor	101
3.13 Electrical Field	67	4.14 Alternating-Current Motor Types	101
3.14 Discharging a Capacitor.....	68	4.15 Reversing the Rotation of an Alternating-Current Motor.....	102
3.15 Determining Capacitance.....	68	Part B—Transformers	102
3.16 Uses of Capacitors.....	69	4.16 Transformer Basics	102
3.17 Phase Relationship	69	4.17 Secondary Induced Voltage	103
Part C—Induction.....	70	4.18 Efficiency	103
3.18 Self-Induction	71	4.19 Transformer Turns Ratio	104
3.19 Induced Voltage and Applied Current.....	71	4.20 Autotransformers	106
3.20 Conductor Alternating-Current Resistance.....	72	4.21 Power Losses	106
3.21 Conductor Shape	72	4.22 Transformer kVA Rating.....	108
3.22 Magnetic Cores.....	73	4.23 Current Flow.....	108
3.23 Self-Induced and Applied Voltage.....	74	4.24 Current Rating	108
3.24 Inductive Reactance.....	75	Conclusion to Unit 4.....	109
3.25 Phase Relationship	75	Practice Questions for Unit 4	110
3.26 Uses of Induction	75	Challenge Questions for Unit 4.....	115
Part D—Power Factor	75		
3.27 Apparent Power (Volt-Amperes)	76		
3.28 True Power (Watts).....	76		
3.29 Power Factor	77		
3.30 Unity Power Factor.....	77		
3.31 Power Factor Formulas	77		
3.32 Cost of True Power	78		
3.33 Effects of Power Factor	79		
Part E—Efficiency.....	80		
3.34 Efficiency Formulas.....	81		
Conclusion to Unit 3.....	82		
Practice Questions for Unit 3	83		
Challenge Questions for Unit 3.....	91		
		CHAPTER 2—NEC CALCULATIONS (Essential for Journeyman and Master's Licensing Exams)	119
		UNIT 5—RACEWAY AND BOX CALCULATIONS	121
		Part A—Raceway Fill	121
		5.1 Understanding the <i>NEC</i> , Chapter 9 Tables	121
		5.2 Raceway Calculations	131
		5.3 Wireways	132
		5.4 Tips for Raceway Calculations	135
		Part B—Outlet Box Fill Calculations [314.16]	135
		5.5 Sizing Box—Conductors All the Same Size [Table 314.16(A)]	135

5.6 Conductor Equivalents	136
5.7 Outlet Box Sizing [314.16(B)]	139
Part C—Pull Boxes, Junction Boxes, and Conduit Bodies	141
5.8 Pull/Junction Box Sizing Requirements	142
5.9 Pull/Junction Box Sizing Tips	144
5.10 Pull Box Examples	144
Summary.....	146
Conclusion to Unit 5.....	146
Practice Questions for Unit 5	147
Challenge Questions for Unit 5.....	152
 UNIT 6—CONDUCTOR SIZING AND PROTECTION CALCULATIONS 155	
Part A—General Conductor Requirements.....	155
6.1 Conductor Insulation [Table 310.104(A)].....	155
6.2 Conductor Sizing [110.6]	158
6.3 Smallest Conductor Size [310.106(A)].....	159
6.4 Conductor Size—Terminal Temperature Rating [110.14(C)]....	159
6.5 Conductors in Parallel	161
6.6 <i>NEC</i> Requirements for Conductors in Parallel [310.10(H)].....	163
6.7 Overcurrent Protection [Article 240]	165
6.8 Overcurrent Protection of Conductors—General Requirements [240.4].....	167
6.9 Overcurrent Protection of Conductors—Specific Requirements... 171	
Part B—Conductor Ampacity.....	185
6.10 Conductor Ampacity.....	185
6.11 Ambient Temperature Correction Factors [Table 310.15(B)(2)(a)]	186
6.12 Conductor Bundling Ampacity Adjustment Factors [Table 310.15(B)(3)(a)]	190
6.13 Ambient and Conductor Bundling Adjustment.....	193
6.14 Current-Carrying Conductors	195
6.15 Wireway Conductor Ampacity [376.22(B)]	197
6.16 Conductor Sizing Summary.....	197
Part C—Article 690 Solar PV systems	198
6.17 Maximum Voltage [690.7].....	198
6.18 Circuit Sizing and Protection [690.8]	202
6.19 Overcurrent Protection [690.9].....	209
Conclusion to Unit 6.....	211
Practice Questions for Unit 6	212
Challenge Questions for Unit 6	218
 UNIT 7—MOTOR AND AIR-CONDITIONING CALCULATIONS 223	
Part A—Motor Calculations	223
7.1 Scope of Article 430.....	223
7.2 FLC versus Motor Nameplate	224
7.3 Highest Rated Motor [430.17]	226
7.4 Branch-Circuit Conductor Size	226
7.5 Feeder Conductor Size [430.24].....	229
7.6 Overload Protection [430.6(A)(2) and 430.32(A)]	230
7.7 Branch-Circuit Short-Circuit and Ground-Fault Protection [430.51].....	236
7.8 Branch-Circuit Summary	239
7.9 Feeder Protection [430.62]	240
7.10 Motor VA Calculations	241
Part B—Air-Conditioning Calculations	243
7.12 Scope of Article 440.....	243
7.13 Other Articles	243
7.14 Short-Circuit and Ground-Fault Protection.....	244
7.15 Conductor Sizing for a Single Motor-Compressor	245
Conclusion to Unit 7.....	246
Practice Questions for Unit 7	247
Challenge Questions for Unit 7	251
 UNIT 8—VOLTAGE-DROP CALCULATIONS 253	
Part A—Conductor Resistance Calculations.....	253
8.1 Conductor Resistance	253
8.2 Conductor Resistance—Direct-Current Circuits [Chapter 9, Table 8]	256
8.3 Conductor Resistance—Alternating-Current Circuits.....	257
8.4 Alternating-Current Resistance	257
8.5 Alternating-Current Resistance as Compared to Direct-Current Resistance.....	259
Part B—Voltage-Drop Considerations	260
8.6 <i>NEC</i> Voltage-Drop Recommendations.....	260
8.7 Determining Circuit Conductors' Voltage Drop—Ohm's Law Method.....	262
8.8 Determining Circuit Conductors' Voltage Drop—Formula Method	262
8.9 Sizing Conductors to Prevent Excessive Voltage Drop	264
8.10 Limiting Conductor Length to Minimize Voltage Drop.....	265
8.11 Limiting Current to Limit Voltage Drop.....	267
Conclusion to Unit 8.....	268
Practice Questions For Unit 8	269
Challenge Questions For Unit 8	275
 UNIT 9—DWELLING UNIT CALCULATIONS 277	
Part A—General Requirements	277
9.1 General Requirements	277
9.2 Voltages [220.5(A)]	278
9.3 Fraction of an Ampere [220.5(B)]	278

Table of Contents

9.4 Lighting and Receptacles	279
9.5 Cooking Equipment—Branch Circuit [Table 220.55, Note 4]....	280
Part B—Standard Method—Feeder/Service Load Calculations	283
9.6 Dwelling Unit Feeder/Service Load Calculations (Article 220, Part III)	283
9.7 Dwelling Unit Example	286
Part C—Optional Method—Feeder/Service Load Calculations..	292
9.8 Dwelling Unit Optional Calculations [220.82].....	292
9.9 Optional Calculation Example	293
Part D—Other Topics of Interest.....	294
9.10 Neutral Calculations [220.61].....	294
9.11 Grounding and Bonding of Service Equipment.....	297
Conclusion to Unit 9.....	301
Practice Questions for Unit 9	302
Challenge Questions For Unit 9	309
 CHAPTER 3—ADVANCED NEC CALCULATIONS (Essential for Master’s Exams).....	313
 UNIT 10—MULTIFAMILY DWELLING CALCULATIONS	315
10.1 Multifamily Dwelling Calculations—General.....	316
10.2 Multifamily Dwelling Calculation Examples— Standard Method.....	317
Part A—Standard Method—Feeder/Service Load Calculations	317
10.3 Multifamily Dwelling Calculations—Standard Method Example	325
Part B—Optional Method—Feeder/Service Load Calculations ..	327
10.4 Multifamily Dwelling Unit Calculations [220.84]— Optional Method.....	327
10.5 Multifamily—Optional Method Example 1 [220.84]	327
10.6 Multifamily—Optional Method Example 2 [220.84]	330
10.7 Two-Family Dwelling Units [220.85].....	331
Conclusion to Unit 10.....	334
Practice Questions for Unit 10	335
Challenge Questions for Unit 10	340
 UNIT 11—COMMERCIAL CALCULATIONS.....	343
Part A—General	343
11.1 General Requirements	343
11.2 Conductor Ampacity [Article 100].....	343
11.3 Conductor Overcurrent Protection [240.4]	345
11.4 Voltages [220.5(A)]	347
11.5 Fractions of an Ampere [220.5(B)].....	347
11.6 Lighting—Demand Factors [Tables 220.12 and 220.42]	347
11.7 Lighting Without Demand Factors [215.2(A) (1), 230.42(A)(1), and Table 220.12]	349
11.8 Sign Circuit [220.14(F) and 600.5]	350
11.9 Lighting—Miscellaneous	351
11.10 Multioutlet Receptacle Assembly [220.14(H)]	351
11.11 Receptacle VA Load	353
11.12 Banks and Offices—General Lighting and Receptacles [220.14(K)]	354
Part B—Examples	356
11.13 Bank/Office Building Example	356
11.14 Mobile/Manufactured Home Park [550.31].....	358
11.15 Recreational Vehicle Park [551.73].....	359
11.16 Marina [555.12].....	360
Part C—Optional Method—Feeder/Service Load Calculations.....	361
11.17 New Restaurant—Optional Method [220.88]	361
Part D—Welders	362
11.18 Arc Welders	362
11.19 Resistance Welders.....	364
11.20 Light Industrial Calculation.....	365
Conclusion to Unit 11.....	367
Practice Questions for Unit 11	368
Challenge Questions for Unit 11	371
 UNIT 12—TRANSFORMER CALCULATIONS	373
Part A—General	373
12.1 Transformer Basics	374
12.2 Secondary Induced Voltage	374
12.3 Autotransformers	375
12.4 Power Losses	376
12.5 Efficiency	377
12.6 Delta/Delta Connected Transformers	378
12.7 Delta/Wye Connected Transformers	381
12.8 Transformer Turns Ratio	382
12.9 Transformer kVA Rating	384
12.10 Current Flow	384
12.11 Line Currents	385
Part B—NEC Requirements	388
12.12 Transformer Overcurrent Protection	388
12.13 Primary Conductor Sizing	390
12.14 Secondary Conductor Sizing	391
12.15 Grounding and Bonding	394
Conclusion to Unit 12.....	397
Practice Questions for Unit 12	398
Challenge Questions for Unit 12	402

CHAPTER 4—MOTOR CONTROL BASICS (Journeyman and Master’s Exams in Some States)	405
UNIT 13—MOTOR CONTROL BASICS	407
Part A Basic Motor Control Concepts	407
13.1 Motor Control Language	408
13.2 Motor Control Basics.....	411
13.3 Reading a Motor Control Schematic.....	411
Part B Motor Control Circuits	413
13.4 2-Wire Control Circuits.....	413
13.5 3-Wire Control Circuits.....	416
13.6 3-Wire Circuit in a Wiring (Connection) Diagram.....	419
13.7 Multiple Start-Stop Pushbutton Stations.....	420
13.8 Reversing Three-Phase Motors	423
13.9 Forward and Reverse Contactors	424
13.10 Interlocking Devices.....	424
13.11 Electrical Interlock for Magnetic Reversing Controls	426
Conclusion to Unit 13.....	428
Practice Questions for Unit 13	429
Challenge Questions for Unit 13.....	432

CHAPTER 5—NEC PRACTICE QUESTIONS (Essential for all Journeyman and Master’s Exams)	435
Practice Quizzes	
Practice Quiz 1—Straight Order [90–210.8]	437
Practice Quiz 1—Random Order [90–210.8].....	446
Practice Quiz 2—Straight Order [210.8–240.54]	451
Practice Quiz 2—Random Order [90.2–240.60].....	460
Practice Quiz 3—Straight Order [240.60–300.8]	465
Practice Quiz 3—Random Order [90.3–300.6].....	474
Practice Quiz 4—Straight Order [300.9–344.10]	479
Practice Quiz 4—Random Order [90.2–342.26].....	488
Practice Quiz 5—Straight Order [344.10–404.9]	493
Practice Quiz 5—Random Order [215.10–404.8].....	502
Practice Quiz 6—Straight Order [404.9–430.87]	507
Practice Quiz 6—Random Order [210.21–430.81].....	516
Practice Quiz 7—Straight Order [430.103–514.11]	521
Practice Quiz 7—Random Order [100–514.11].....	530
Practice Quiz 8—Straight Order [514.13–647.4]	535
Practice Quiz 8—Random Order [200.6–640.4].....	544
Practice Quiz 9—Straight Order [647.4–700.12]	549
Practice Quiz 9—Random Order [100–690.49].....	559
Practice Quiz 10—Straight Order [700.15–Chapter 9]	564
Practice Quiz 10—Random Order [220.82–Chapter 9].....	573
NEC Challenge Quizzes	
Challenge Quiz 1—Article 90 through Chapter 9	579
Challenge Quiz 2—Article 90 through Chapter 9.....	588
Challenge Quiz 3—Article 90 through Chapter 9.....	597
Challenge Quiz 4—Article 90 through Chapter 9.....	606
Challenge Quiz 5—Article 90 through Chapter 9	616
Challenge Quiz 6—Article 90 through Chapter 9	625
Challenge Quiz 7—Article 90 through Chapter 9	634
Final NEC Exams	
Final Exam 1—Questions in Random Order for Article 90 through Annex C.....	643
Final Exam 2—Questions in Random Order for Article 90 through Annex C.....	652