

# Table of Contents

<b>Introduction</b> .....	x
<b>How to Use This Textbook</b> .....	xi
<b>About the Author</b> .....	xii
<b>About the Graphic Illustrator</b> .....	xiii
<b>Mike Holt Enterprises Team</b> .....	xiv

## **CHAPTER 1—ELECTRICAL FUNDAMENTALS** .....

1

### **Unit 1—Matter** .....

3

<b>Introduction</b> .....	3
1.1 Matter .....	3
1.2 Atomic Theory.....	3
1.3 Law of Electrical Charges .....	4
1.4 Law of Atomic Charges .....	4
1.5 Charged Material (Static Charge) .....	5
1.6 Neutralizing a Charge .....	6
1.7 Lightning .....	6
1.8 Lightning Protection.....	7
<b>Summary</b> .....	9
<b>Conclusion</b> .....	10
<b>Practice Questions</b> .....	11

### **Unit 2—Electron Theory**.....

15

<b>Introduction</b> .....	15
2.1 Electron Orbits.....	15
2.2 Valence Electrons.....	15
2.3 Freeing Electrons from an Atom .....	16
2.4 Conductors .....	16
2.5 Insulators.....	16
2.6 Semiconductors.....	16
2.7 Atomic Bonding .....	17
2.8 Compounds .....	17
<b>Summary</b> .....	19
<b>Conclusion</b> .....	20
<b>Practice Questions</b> .....	21

### **Unit 3—Magnetism**.....

23

<b>Introduction</b> .....	23
3.1 The Natural Magnet .....	23
3.2 Magnetic Polarities .....	23
3.3 Magnetic Compass .....	23
3.4 Magnetic Molecule .....	24
3.5 Magnetic Properties.....	24
3.6 How to Magnetize Iron .....	24
3.7 Permanent and Temporary Magnets.....	24
3.8 Demagnetizing Magnets .....	24
3.9 Magnetic Lines of Force.....	25
3.10 Magnetic Materials .....	25
3.11 Law of Attraction and Repulsion.....	25
3.12 Retentivity .....	26
3.13 Permeability.....	26
<b>Summary</b> .....	27
<b>Conclusion</b> .....	28
<b>Practice Questions</b> .....	29

### **Unit 4—Electricity**.....

31

<b>Introduction</b> .....	31
4.1 Electric Current Flow (Electricity).....	31
4.2 Electricity.....	31
4.3 Useful Purposes of Electricity .....	34
4.4 Dangers of Electricity.....	37
4.5 <i>National Electrical Code</i> .....	39
<b>Summary</b> .....	41
<b>Conclusion</b> .....	43
<b>Practice Questions</b> .....	44

### **Unit 5—Electromagnetism** .....

47

<b>Introduction</b> .....	47
5.1 Electromagnetism in a Wire .....	47
5.2 Field Intensity .....	47
5.3 Field Interaction .....	47
5.4 Field Interaction of Loops .....	48

5.5 Electromagnetism in a Coil .....	48	8.6 Percent Increase.....	84
5.6 Magnetic Core .....	49	8.7 Reciprocals.....	85
5.7 Amperes and Turns .....	49	8.8 Squaring a Number.....	86
<b>Summary</b> .....	50	8.9 Square Root.....	87
<b>Conclusion</b> .....	50	8.10 Volume .....	88
<b>Practice Questions</b> .....	51	8.11 Kilo.....	88
 		8.12 Rounding Off.....	89
<b>Unit 6—Uses of Electromagnetism</b> .....	53	8.13 Parentheses.....	89
<b>Introduction</b> .....	53	8.14 Testing Your Answer for Reasonableness.....	90
6.1 Basic Electric Meters .....	53	<b>Summary</b> .....	91
6.2 Electric Motors .....	56	<b>Conclusion</b> .....	92
6.3 Electrical Generators.....	58	<b>Practice Questions</b> .....	93
6.4 Electromagnetic Relay .....	58	 	
<b>Summary</b> .....	61	<b>Unit 9—Electrical Formulas</b> .....	97
<b>Conclusion</b> .....	63	<b>Introduction</b> .....	97
<b>Practice Questions</b> .....	64	9.1 Electrical Circuit.....	97
 		9.2 Power Source .....	97
<b>Chapter 1 Final Exam Questions</b> .....	67	9.3 Conductance .....	98
 		9.4 Circuit Resistance .....	98
<b>CHAPTER 2—BASIC ELECTRICITY</b> .....	73	9.5 Ohm’s Law .....	99
<b>Unit 7—The Electrical Circuit</b> .....	75	9.6 Ohm’s Law and Alternating Current.....	99
<b>Introduction</b> .....	75	9.7 Ohm’s Law Formula Circle .....	100
7.1 The Electrical Circuit .....	75	9.8 PIE Formula Circle.....	102
7.2 Electron Current Flow Theory .....	76	9.9 Formula Wheel .....	102
7.3 Conventional Current Flow Theory.....	76	9.10 Using the Formula Wheel .....	103
7.4 Voltage (Pressure).....	76	9.11 Power Losses of Conductors .....	104
7.5 Resistance.....	77	9.12 Cost of Power .....	104
7.6 Electric Current.....	78	9.13 Power Changes with the Square of the Voltage .....	105
7.7 Power .....	78	<b>Summary</b> .....	109
7.8 Electrical Formulas .....	78	<b>Conclusion</b> .....	110
<b>Summary</b> .....	79	<b>Practice Questions</b> .....	111
<b>Conclusion</b> .....	80	 	
<b>Practice Questions</b> .....	81	<b>Chapter 2 Final Exam Questions</b> .....	115
<b>Unit 8—Math</b> .....	83	<b>CHAPTER 3—BASIC ELECTRICAL</b>	
<b>Introduction</b> .....	83	<b>CIRCUITS</b> .....	121
8.1 Whole Numbers .....	83	<b>Unit 10—Series Circuits</b> .....	123
8.2 Decimals .....	83	<b>Introduction</b> .....	123
8.3 Fractions.....	83	10.1 Practical Uses of the Series Circuit.....	123
8.4 Percentages.....	83	10.2 Understanding Series Calculations .....	124
8.5 Multiplier .....	84	10.3 Series Circuit Calculations .....	127
		10.4 Power Calculations .....	128

10.5 Variations.....	128
10.6 Series Circuit Notes .....	128
10.7 Series-Connected Power Supplies .....	128
<b>Summary</b> .....	130
<b>Conclusion</b> .....	131
<b>Practice Questions</b> .....	132
<b>Unit 11—Parallel Circuits</b> .....	135
<b>Introduction</b> .....	135
11.1 Practical Uses of the Parallel Circuits .....	135
11.2 Understanding Parallel Calculations .....	137
11.3 Circuit Resistance .....	138
11.4 Parallel Circuit Notes.....	140
11.5 Parallel-Connected Power Supplies.....	141
<b>Summary</b> .....	142
<b>Conclusion</b> .....	143
<b>Practice Questions</b> .....	144
<b>Unit 12—Series-Parallel Circuits</b> .....	145
<b>Introduction</b> .....	145
12.1 Review of Series and Parallel Circuits .....	145
12.2 Working With Series-Parallel Circuits.....	146
12.3 Voltage .....	147
<b>Summary</b> .....	148
<b>Conclusion</b> .....	148
<b>Practice Questions</b> .....	149
<b>Unit 13—Multiwire Circuits</b> .....	151
<b>Introduction</b> .....	151
13.1 Neutral Conductor.....	151
13.2 Grounded Conductor .....	152
13.3 Current Flow on the Neutral Conductor .....	152
13.4 Balanced Systems .....	153
13.5 Unbalanced Current.....	153
13.6 Multiwire Branch Circuits.....	155
13.7 Dangers of Multiwire Circuits .....	156
13.8 <i>NEC</i> Requirements.....	157
<b>Summary</b> .....	159
<b>Conclusion</b> .....	160
<b>Practice Questions</b> .....	161
<b>Chapter 3 Final Exam Questions</b> .....	165

<b>CHAPTER 4—ELECTRICAL SYSTEMS AND PROTECTION</b> .....	171
<b>Unit 14—The Electrical System</b> .....	173
<b>Introduction</b> .....	173
14.1 Current Flow .....	173
14.2 Utility Neutral Current Path.....	173
14.3 Utility Ground-Fault Current Path.....	174
14.4 Premises Neutral Current Path .....	174
14.5 Premises Ground-Fault Current Path .....	174
14.6 Utility High-Voltage Transmission Lines .....	175
14.7 Conductor Voltage Drop .....	175
14.8 Conductor Power Loss .....	176
14.9 Reducing Voltage Drop and Power Loss .....	177
14.10 Generating Plants .....	177
14.11 Step-Up Substation at Generating Plant .....	177
14.12 Transmission Line .....	178
14.13 Step-Down Substation .....	178
14.14 Primary Distribution Feeders.....	178
14.15 Distribution Transformer.....	178
14.16 Secondary Distribution Line .....	178
<b>Summary</b> .....	180
<b>Conclusion</b> .....	181
<b>Practice Questions</b> .....	182
<b>Unit 15—Protection Devices</b> .....	185
<b>Introduction</b> .....	185
<b>Part A—Overcurrent Protection Devices</b> .....	185
15.1 Overcurrent Protection .....	185
15.2 Clearing Faults.....	186
15.3 Overcurrent Protection Device Types.....	187
15.4 Fuse .....	187
15.5 Circuit Breaker Trip Elements .....	188
15.6 Circuit Breaker Types.....	188
15.7 Available Short-Circuit Current.....	189
15.8 Interrupting Rating .....	189
15.9 Short-Circuit Current Rating.....	190
15.10 Current-Limiting Protection.....	190
<b>Part B— Ground-Fault Circuit Interrupters</b> .....	191
15.11 How a GFCI Works .....	191
15.12 Neutral-to-Case Detection .....	192
15.13 Line-to-Neutral Shock Hazard.....	192

15.14 GFCI Fails—Circuit Remains Energized .....	192	17.5 Uses of Capacitors .....	226
15.15 GFCI Test Button .....	193	17.6 Phase Relationship .....	227
<b>Part C—Arc-Fault Circuit Interrupters</b> .....	193	<b>Summary</b> .....	228
15.16 Arcing Definition .....	193	<b>Conclusion</b> .....	229
15.17 Series versus Parallel Arc .....	193	<b>Practice Questions</b> .....	230
15.18 AFCIs and the <i>NEC</i> .....	194	<b>Unit 18—Induction</b> .....	233
15.19 AFCIs—How They Operate .....	194	<b>Introduction</b> .....	233
<b>Part D—Ground-Fault Protection of Equipment</b> .....	194	18.1 Self-Induction .....	233
15.20 Ground-Fault Protection of Equipment Definition .....	194	18.2 Induced Voltage and Applied Current .....	234
<b>Summary</b> .....	195	18.3 Conductor AC Resistance .....	234
<b>Conclusion</b> .....	197	18.4 Impedance .....	235
<b>Practice Questions</b> .....	198	18.5 Conductor Shape .....	236
<b>Chapter 4 Final Exam Questions</b> .....	203	18.6 Magnetic Cores .....	236
 		18.7 Self-Induced and Applied Voltage .....	237
<b>CHAPTER 5—ALTERNATING CURRENT</b> .....	209	18.8 Current Flow .....	237
<b>Unit 16—Alternating Current</b> .....	211	18.9 Phase Relationship .....	238
<b>Introduction</b> .....	211	18.10 Uses of Induction .....	238
16.1 Current Flow .....	211	<b>Summary</b> .....	240
16.2 Why Alternating Current Is Used .....	211	<b>Conclusion</b> .....	241
16.3 How Alternating Current Is Produced .....	211	<b>Practice Questions</b> .....	242
16.4 AC Generator .....	212	<b>Unit 19—Power Factor and Efficiency</b> .....	245
16.5 Waveform .....	213	<b>Introduction</b> .....	245
16.6 Sine Wave .....	213	<b>Part A—Power Factor</b> .....	245
16.7 Nonsymmetrical Waveform .....	214	19.1 Apparent Power (Volt-Amperes) .....	245
16.8 Frequency .....	214	19.2 True Power (Watts) .....	246
16.9 Phase .....	215	19.3 Power Factor .....	246
16.10 Degrees .....	215	19.4 Unity Power Factor .....	246
16.11 Lead or Lag .....	215	19.5 Power Factor Formulas .....	247
16.12 Values of Alternating Current .....	216	19.6 Cost of True Power .....	248
<b>Summary</b> .....	218	19.7 Effects of Power Factor .....	248
<b>Conclusion</b> .....	219	<b>Part B—Efficiency</b> .....	250
<b>Practice Questions</b> .....	220	19.8 Efficiency .....	250
<b>Unit 17—Capacitance</b> .....	223	19.9 Efficiency Formulas .....	251
<b>Introduction</b> .....	223	<b>Summary</b> .....	253
17.1 Charged Capacitor .....	224	<b>Conclusion</b> .....	254
17.2 Electrical Field .....	224	<b>Practice Question</b> .....	255
17.3 Discharging a Capacitor .....	224	<b>Chapter 5 Final Exam Questions</b> .....	259
17.4 Determining Capacitance .....	225		

## **CHAPTER 6—MOTORS, GENERATORS, AND TRANSFORMERS** ..... 265

### **Unit 20—Motors** ..... 267

#### **Introduction** ..... 267

#### **Part A—Motor Basics** ..... 267

20.1 Motor Principles..... 267

20.2 Dual-Voltage AC Motors ..... 267

20.3 Motor Horsepower Ratings..... 268

20.4 Motor Current Ratings..... 269

20.5 Calculating Motor FLA..... 269

20.6 Motor Starting Current ..... 271

20.7 Motor Running Current..... 271

20.8 Motor Locked-Rotor Current (LRC) ..... 271

20.9 Motor Overload Protection..... 271

#### **Part B—Direct-Current Motors**..... 272

20.10 Direct-Current Motor Principles..... 272

20.11 Direct-Current Motor Types ..... 273

20.12 Reversing the Rotation of a DC Motor..... 273

#### **Part C—Alternating-Current Motors**..... 273

20.13 AC Induction Motor ..... 273

20.14 Alternating-Current Motor Types ..... 274

20.15 Reversing the Rotation of an AC Motor ..... 274

**Summary** ..... 276

**Conclusion**..... 278

**Practice Questions** ..... 279

### **Unit 21—Generators** ..... 283

#### **Introduction** ..... 283

21.1 Direct-Current Generator ..... 283

21.2 Alternating-Current Generator ..... 284

21.3 Three-Phase Generator ..... 284

**Summary** ..... 285

**Conclusion**..... 285

**Practice Questions** ..... 286

### **Unit 22—Transformers** ..... 287

#### **Introduction** ..... 287

22.1 Transformer Basics ..... 287

22.2 Secondary Induced Voltage ..... 287

22.3 Autotransformers ..... 288

22.4 Power Losses ..... 289

22.5 Harmonic Current ..... 290

22.6 Efficiency ..... 291

22.7 Transformer Turns Ratio ..... 291

22.8 Transformer kVA Rating..... 293

22.9 Current Flow ..... 294

22.10 Current Rating ..... 294

**Summary** ..... 296

**Conclusion**..... 297

**Practice Questions** ..... 298

### **Chapter 6 Final Exam Questions**..... 300

## **BASIC ELECTRICAL THEORY CONCLUSION** .. 305

## **BASIC ELECTRICAL THEORY FINAL EXAM** ... 307

## **ANNEX A—GROUNDING AND BONDING** ..... 323

## **INDEX** ..... 345